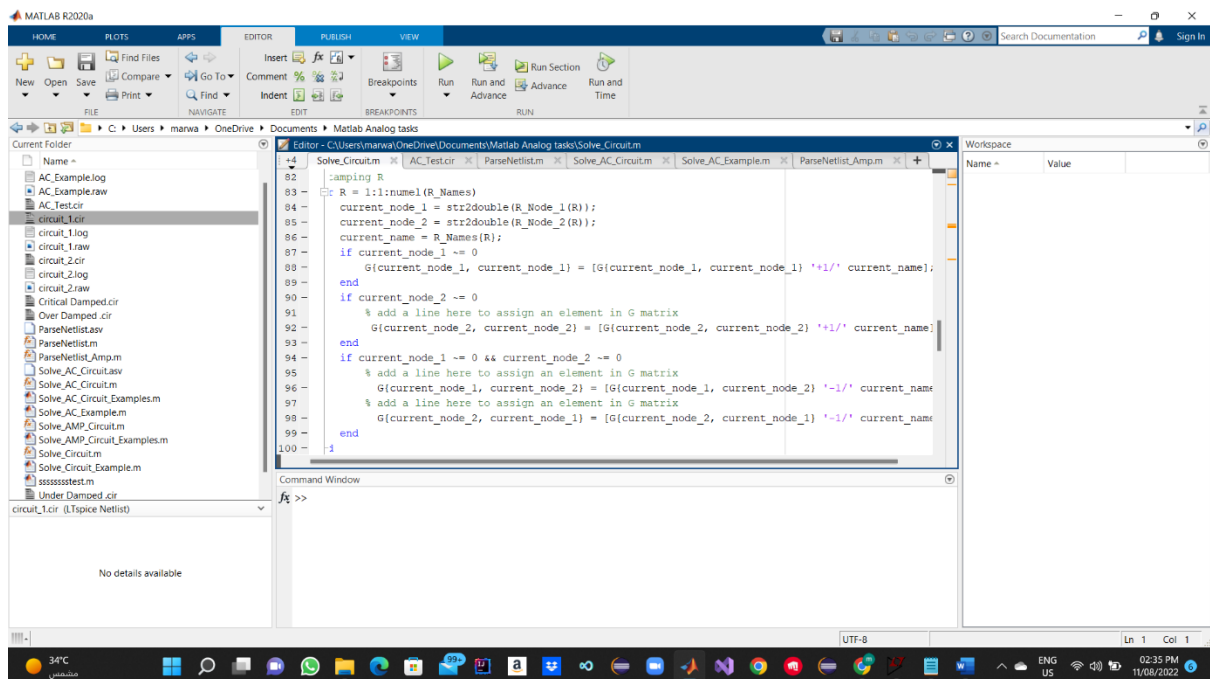


## Part 1 :

Code :



Simulation Results

And Solve Example is completed :

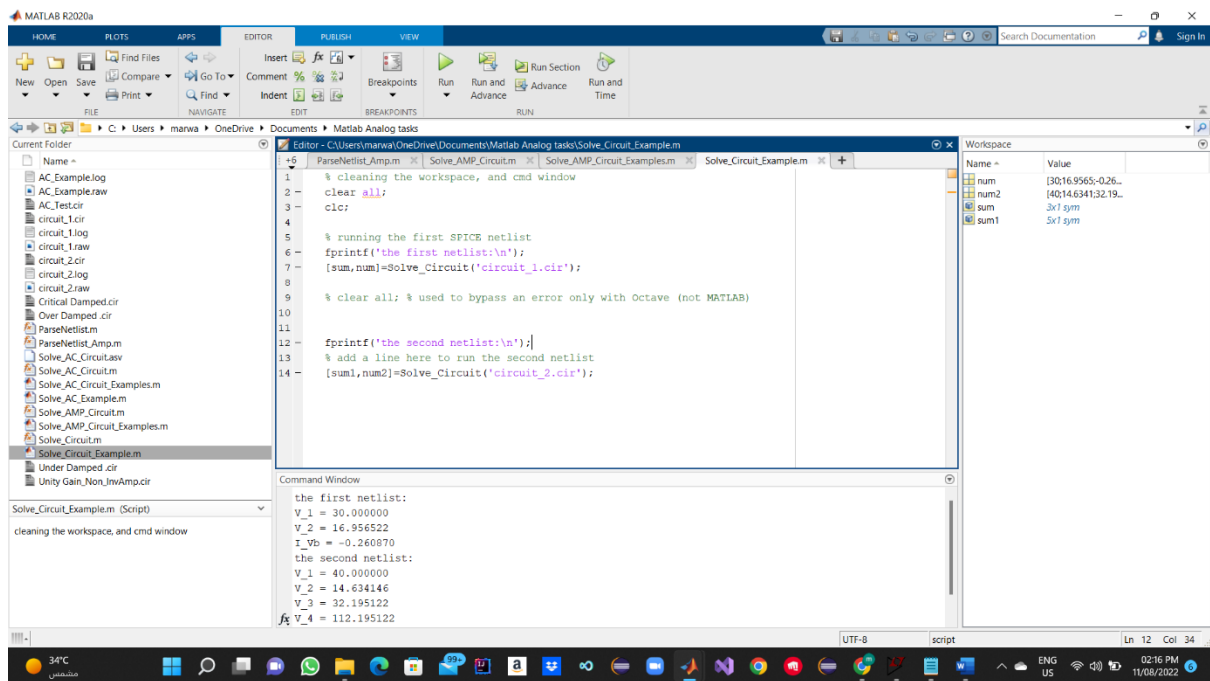


Table Compare:

Matlab	Ltspice
<u>the first netlist:</u> V_1 = 30.000000 V_2 = 16.956522 I_Vb = -0.260870	<u>the first netlist:</u> V(1): 30 voltage V(2): 16.9565 voltage I(Is): 2 device_current
<u>the second netlist:</u> V_1 = 40.000000 V_2 = 14.634146 V_3 = 32.195122 V_4 = 112.195122 I_Vb = -1.268293	<u>the second netlist:</u> I(R3): 1.69565 device_current I(R2): 0.565217 device_current I(R1): 0.26087 device_current I(Vb): -0.26087 device_current  v(1): 40 voltage V(2): 14.6341 voltage V(3): 32.1951 voltage V(4): 112.195 voltage I(Is): 1 device_current I(R6): 0.804878 device_current I(R4): 1.46341 device_current I(R3): -1 device_current I(R2): -0.195122 device_current I(R1): 1.26829 device_current I(Vb): -1.26829 device_current

Ltspice Find The value of the Current in each branch while Its Not Supported in my code And The results of The voltage Nodes My Code have higher precision.

## Part 2:


Created the script for solving Ac.

```

133 % add a line here to assign an element in G matrix
134 G(current_node_1, current_node_2) = [G(current_node_1, current_node_2) '-(i*W)*' curre
135 % add a line here to assign an element in G matrix
136 G(current_node_2, current_node_1) = [G(current_node_2, current_node_1) '-(i*W)*' curre
137 end
138 end
139 % Adding L to The G matrix
140
141
142 for L = 1:1:numel(L_Names)
143     current_node_1 = str2double(L_Node_1(L));
144     current_node_2 = str2double(L_Node_2(L));
145     current_name = L_Names(L);
146     if current_node_1 ~= 0
147         G(current_node_1, current_node_1) = [G(current_node_1, current_node_1) '+ (1/(i*W))]' cur
148     end
149     if current_node_2 ~= 0
150         % add a line here to assign an element in G matrix
151         G(current_node_2, current_node_2) = [G(current_node_2, current_node_2) '+ (1/(i*W))]' cu
152     end
153     if current_node_1 ~= 0 && current_node_2 ~= 0
154         % add a line here to assign an element in G matrix
155         G(current_node_1, current_node_2) = [G(current_node_1, current_node_2) '- (1/(i*W))]' c
156         % add a line here to assign an element in G matrix
157         G(current_node_2, current_node_1) = [G(current_node_2, current_node_1) '- (1/(i*W))]' c
158     end
159 end

```

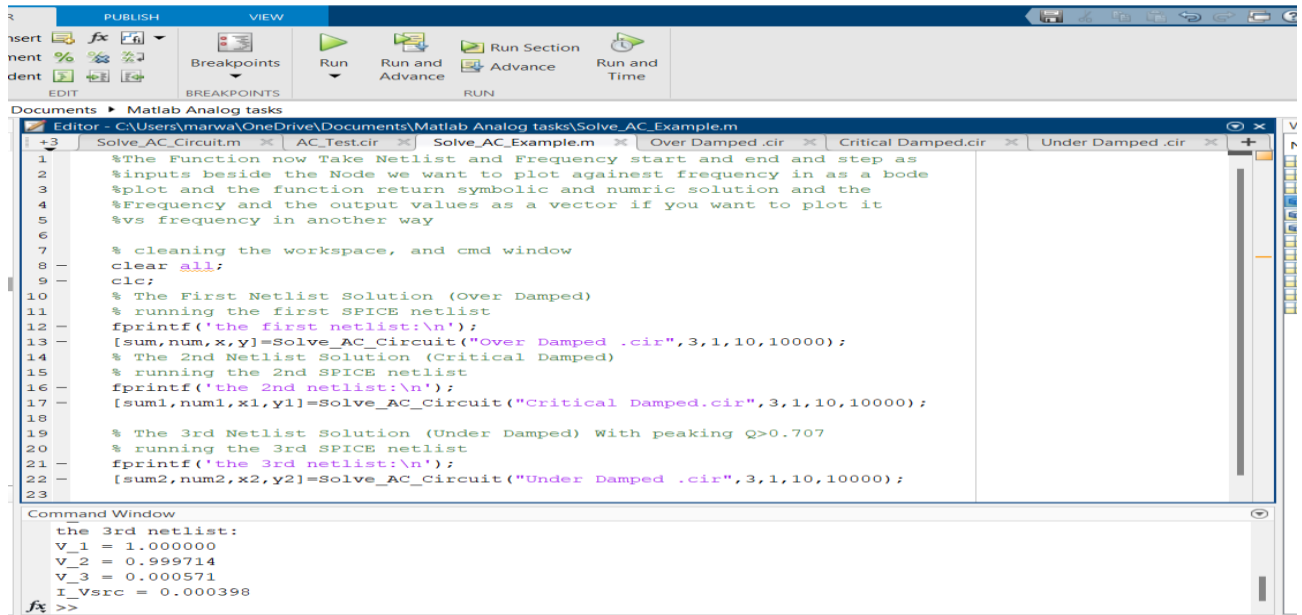Created the script for solving Ac Example.




```
1 %The Function now Take Netlist and Frequency start and end and step as
2 %inputs beside the Node we want to plot against frequency in as a bode
3 %plot and the function return symbolic and numeric solution and the
4 %Frequency and the output values as a vector if you want to plot it
5 %vs frequency in another way
6
7 % cleaning the workspace, and cmd window
8 clear all;
9 clc;
10 % The First Netlist Solution (Over Damped)
11 % running the first SPICE netlist
12 fprintf('the first netlist:\n');
13 [sum,num,x,y]=Solve_AC_Circuit("Over Damped .cir",3,1,10,10000);
14 % The 2nd Netlist Solution (Critical Damped)
15 % running the 2nd SPICE netlist
16 fprintf('the 2nd netlist:\n');
17 [sum1,num1,x1,y1]=Solve_AC_Circuit("Critical Damped.cir",3,1,10,10000);
18
19 % The 3rd Netlist Solution (Under Damped) With peaking Q>0.707
20 % running the 3rd SPICE netlist
21 fprintf('the 3rd netlist:\n');
22 [sum2,num2,x2,y2]=Solve_AC_Circuit("Under Damped .cir",3,1,10,10000);
23
```

Command Window


```
the 3rd netlist:
V_1 = 1.0000000
V_2 = 0.999714
V_3 = 0.000571
I_Vsrc = 0.000398
fx >>
```

## My Simulator Results:


Over Damped RLC:

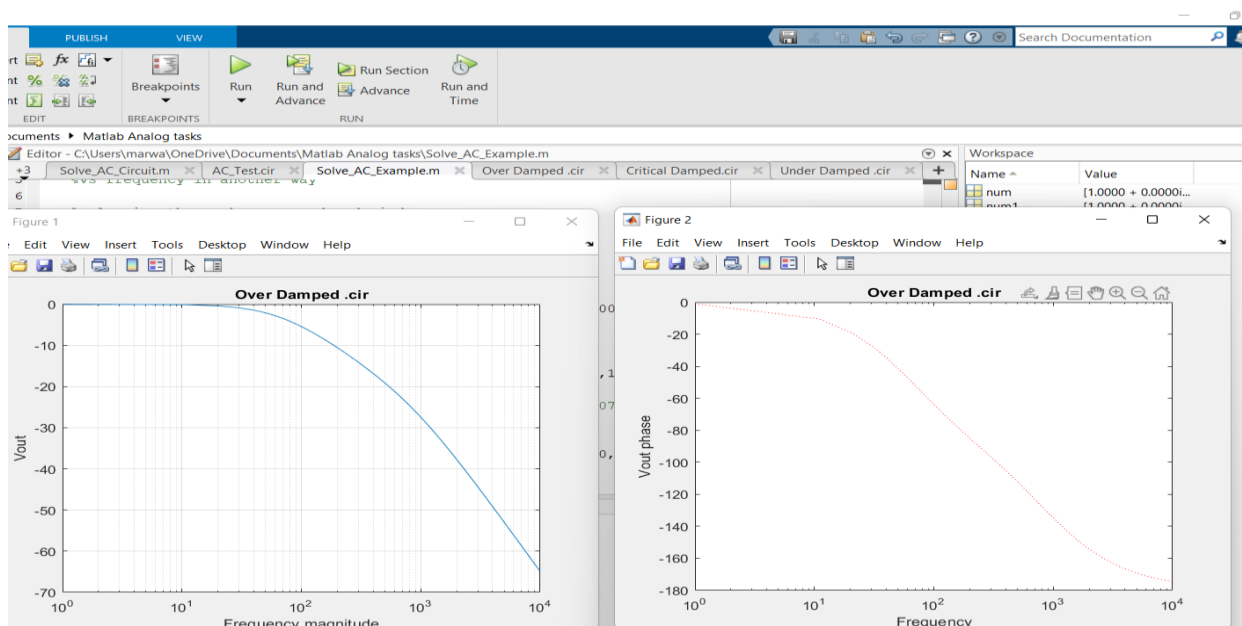


### Over Damped RLC:

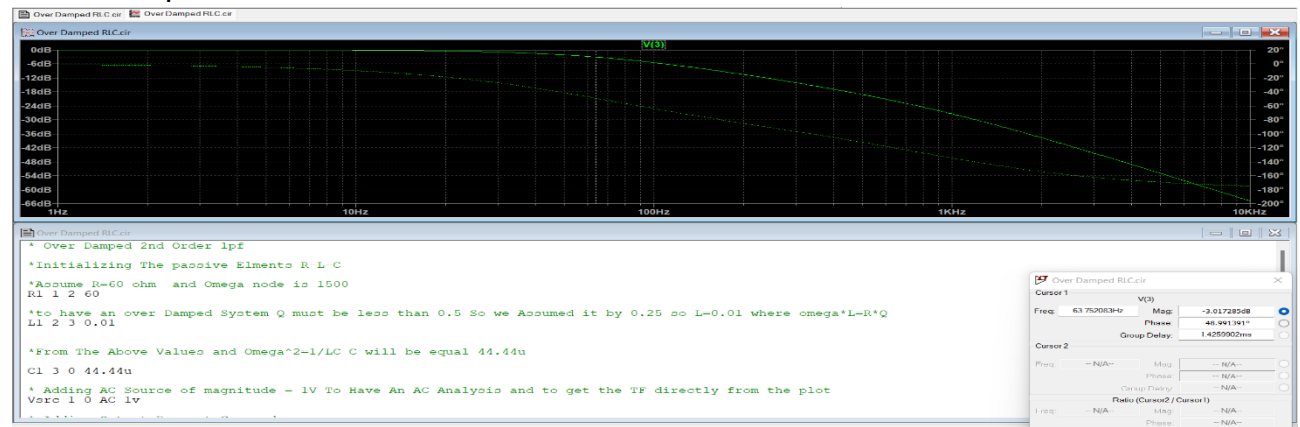

## Critical Damping RLC:

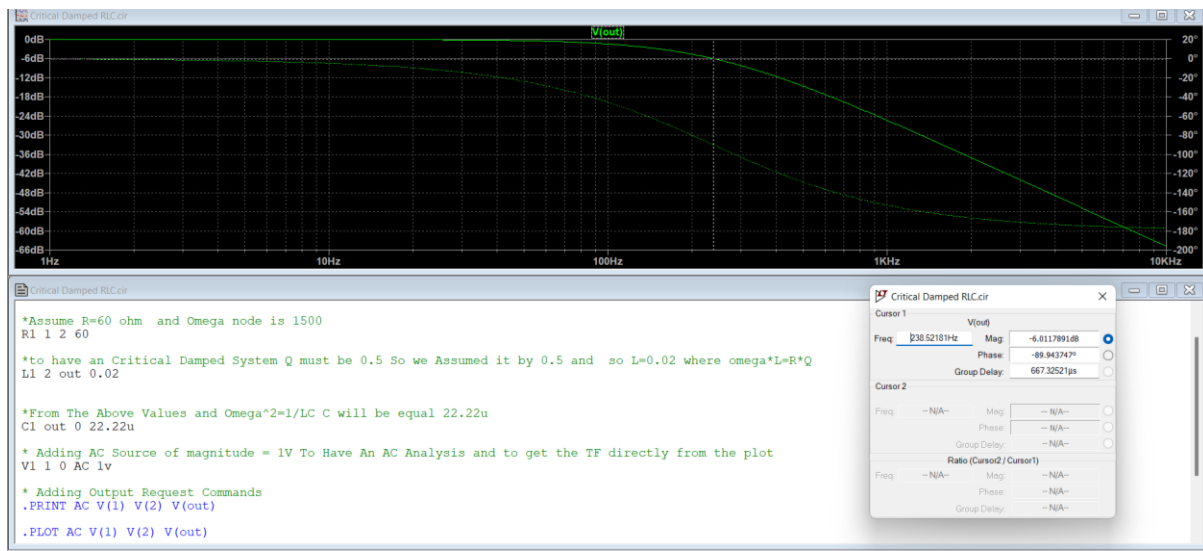

## Under Damped RLC:

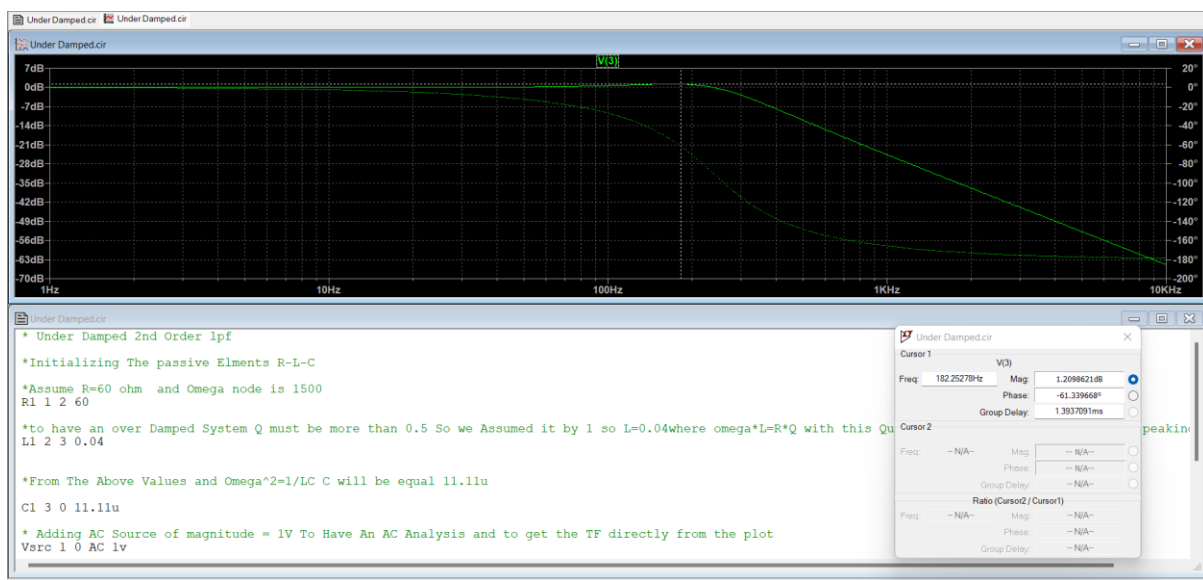


## Comment:

The Graphs Are The Same For Both Lt Spice and my Simulator  
But LtSpice Is faster at getting Results and have more helping tools  
like cursor to have an accurate number for the cutoff Freq etc.

## PART 3:
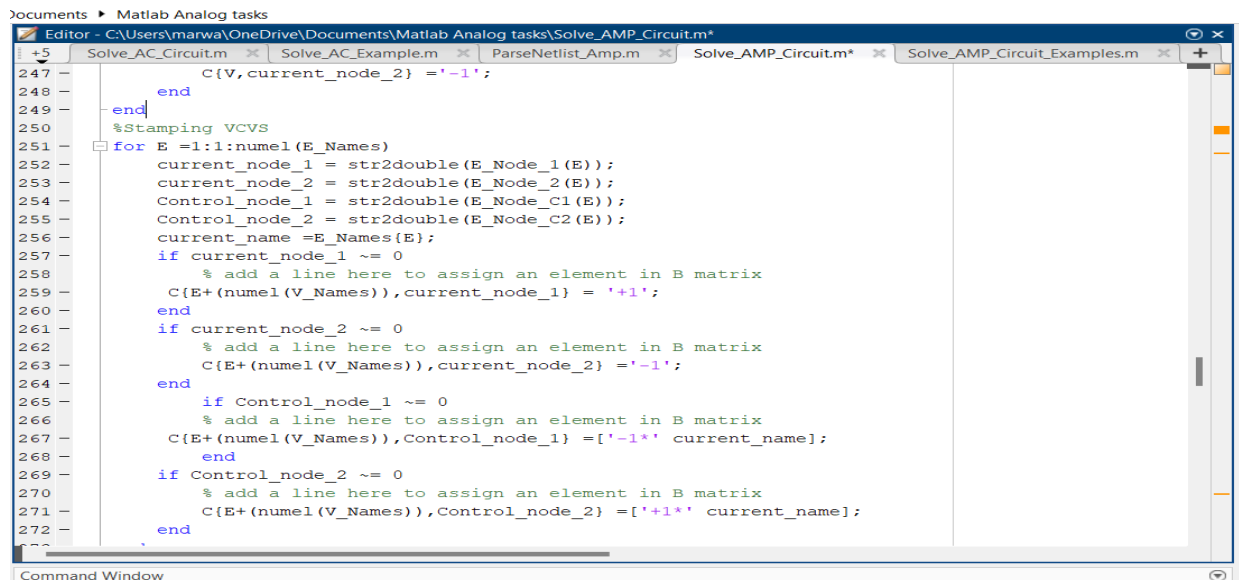
### Added Support for both VCVS and VCCS :




```
247 - C(V,current_node_2) = '-1';
248 -
249 - end
250 - %Stamping VCVS
251 - for E = 1:1:numel(E_Names)
252 -     current_node_1 = str2double(E_Node_1(E));
253 -     current_node_2 = str2double(E_Node_2(E));
254 -     Control_node_1 = str2double(E_Node_C1(E));
255 -     Control_node_2 = str2double(E_Node_C2(E));
256 -     current_name = E_Names(E);
257 -     if current_node_1 ~= 0
258 -         % add a line here to assign an element in B matrix
259 -         C(E+(numel(V_Names)),current_node_1) = '+1';
260 -     end
261 -     if current_node_2 ~= 0
262 -         % add a line here to assign an element in B matrix
263 -         C(E+(numel(V_Names)),current_node_2) = '-1';
264 -     end
265 -     if Control_node_1 ~= 0
266 -         % add a line here to assign an element in B matrix
267 -         C(E+(numel(V_Names)),Control_node_1) = ['-1*' current_name];
268 -     end
269 -     if Control_node_2 ~= 0
270 -         % add a line here to assign an element in B matrix
271 -         C(E+(numel(V_Names)),Control_node_2) = ['-1*' current_name];
272 -     end
273 - end
```
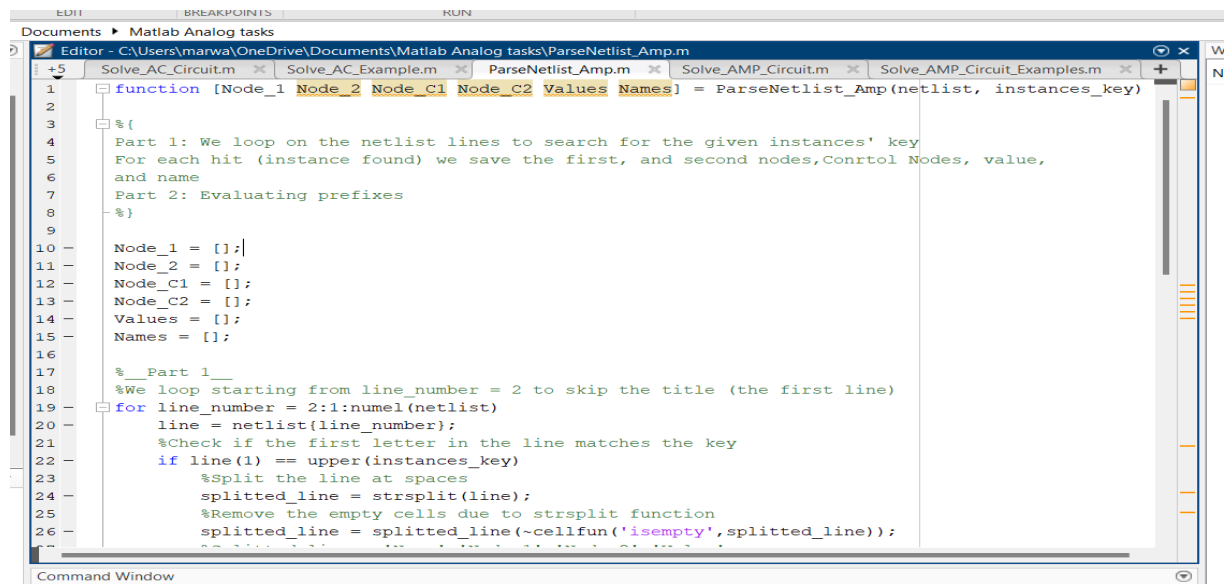
## Note:

Modified The Parseing function to add support for VCVS And VCCS


I used the modifeid one along with the original one ,its not optimum for coding it can be done with the original one with some modifications only.




```
1 - function [Node_1 Node_2 Node_C1 Node_C2 Values Names] = ParseNetlist_Amp(netlist, instances_key)
2 -
3 - %{}
4 - Part 1: We loop on the netlist lines to search for the given instances' key
5 - For each hit (instance found) we save the first, and second nodes,Contrtol Nodes, value,
6 - and name
7 - Part 2: Evaluating prefixes
8 - %{}
9 -
10 - Node_1 = [];
11 - Node_2 = [];
12 - Node_C1 = [];
13 - Node_C2 = [];
14 - Values = [];
15 - Names = [];
16 -
17 - %_Part 1_
18 - %We loop starting from line_number = 2 to skip the title (the first line)
19 - for line_number = 2:1:numel(netlist)
20 -     line = netlist(line_number);
21 -     %Check if the first letter in the line matches the key
22 -     if line(1) == upper(instances_key)
23 -         %Split the line at spaces
24 -         splitted_line = strsplit(line);
25 -         %Remove the empty cells due to strsplit function
26 -         splitted_line = splitted_line(~cellfun('isempty',splitted_line));
```
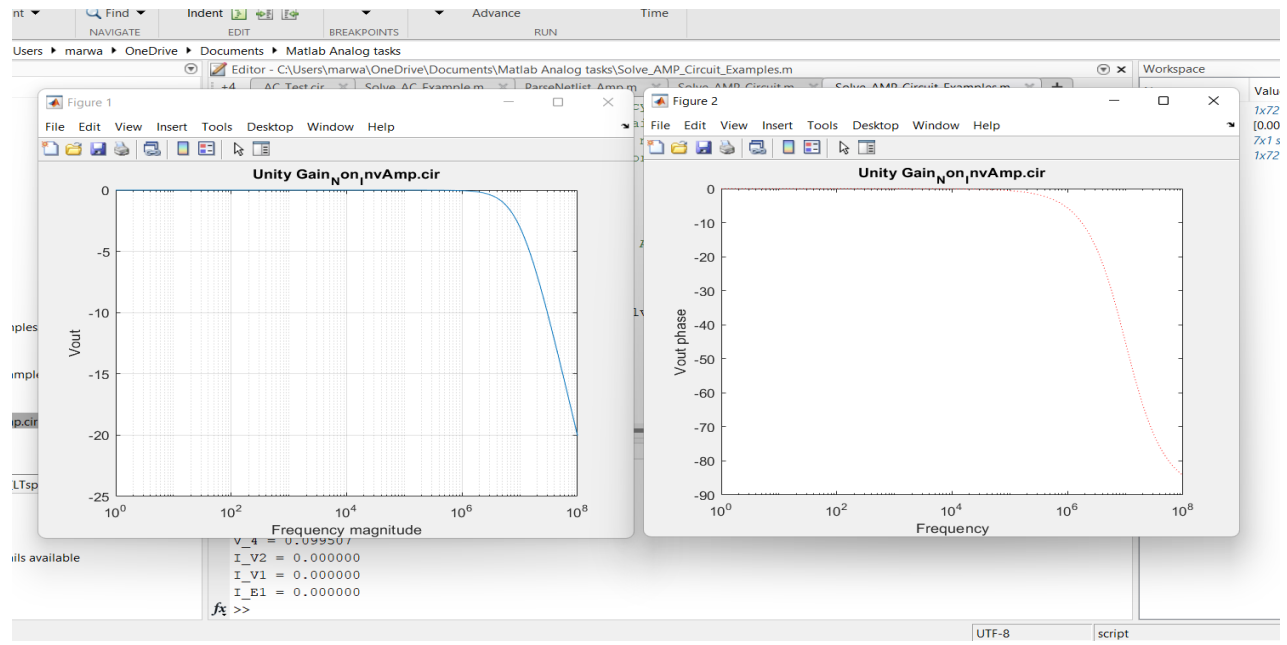
## My Simulator Results :

Non Inverting amplifier with  $UGF=10$  Megahz connected in UGain Configuration



## Lt SPice Results :

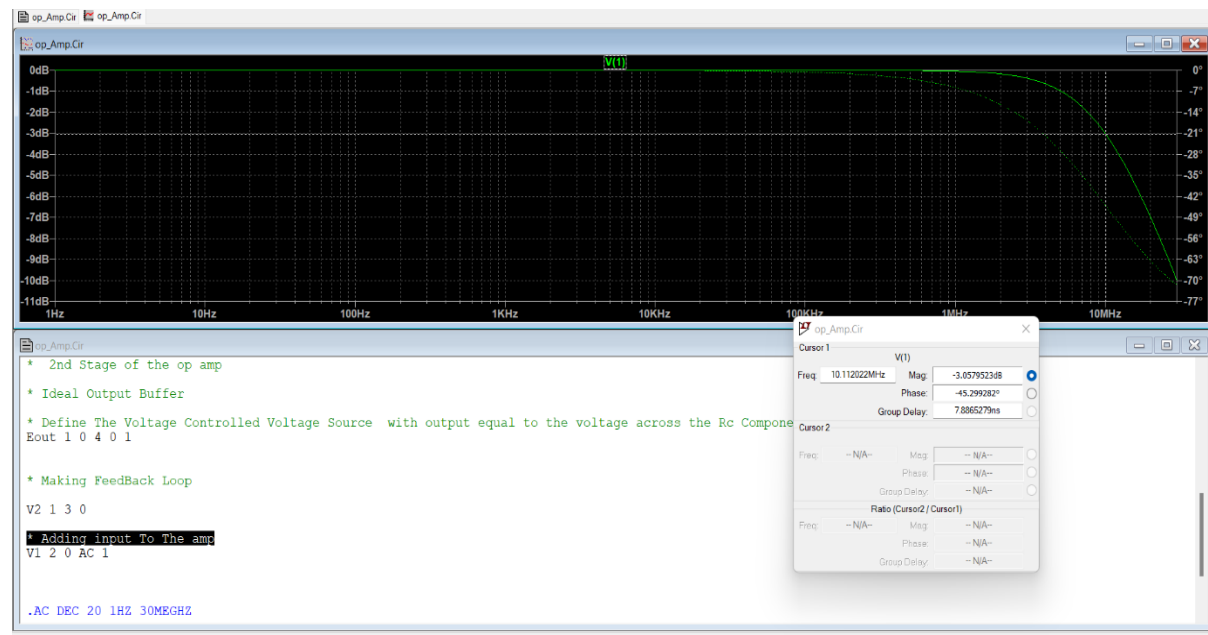

Comment: The Graphs are Identical The Simulator is spice accurate but its much slower than spice.

