

# Analog/Mixed-Signal Simulation and Modeling

## Module 07 Introduction to Phase Locked Loops (PLL)

**Dr. Hesham A. Omran**

Integrated Circuits Laboratory (ICL)  
Electronics and Communications Eng. Dept.  
Faculty of Engineering  
Ain Shams University



# Why PLLs?


- ❑ Practically all digital and radio frequency circuits and most analog/mixed-signal circuits require a precision oscillator
- ❑ Integrated circuit oscillators are not, on their own, suitable for use as frequency- or time-references
  - PVT variations
  - Jitter
- ❑ Insert the oscillator into a phase locked loop where the operating frequency and phase is continuously compared against a precise external time-reference
- ❑ Precise external references are in the 1-200 MHz range
  - Use PLL for synthesizing higher and/or different output frequencies
    - ➔ Clock/Frequency synthesis
  - Other applications exist

# PLL Architecture

## ❑ Negative feedback loop


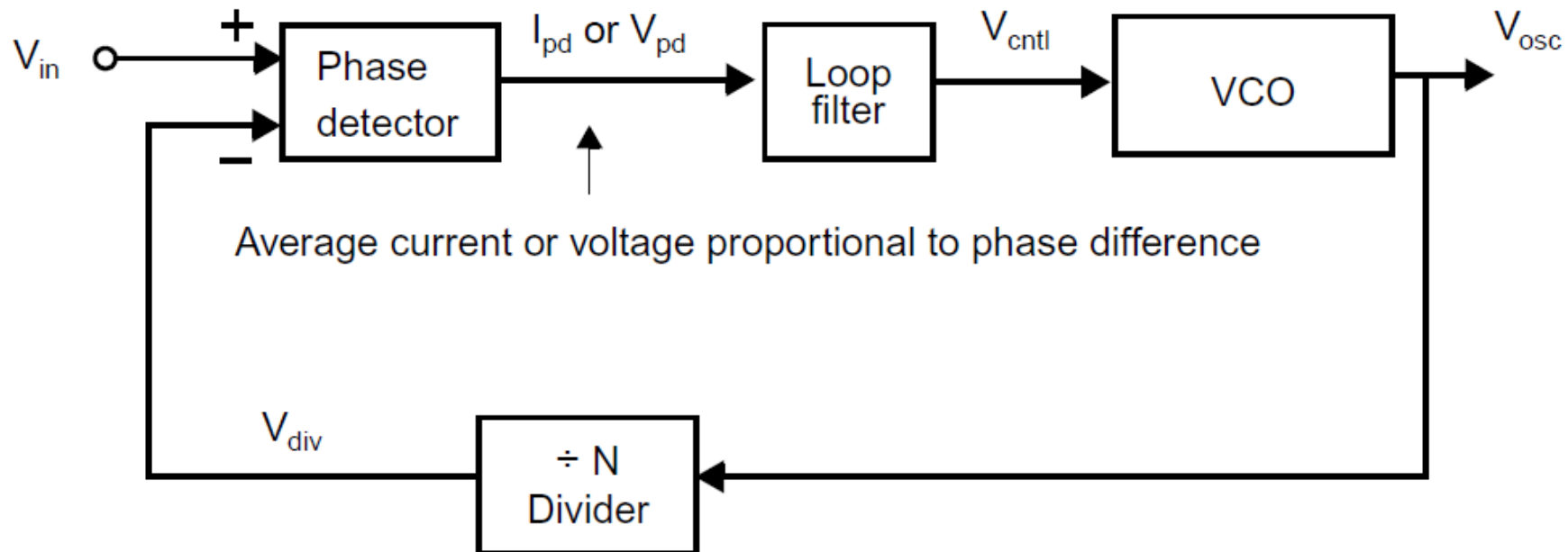
### ■ At steady state: Phase lock condition

- $\phi_{in} - \phi_{fb} = \phi_{err} = \text{constant} \rightarrow \frac{d\phi_{in}}{dt} - \frac{d\phi_{fb}}{dt} = 0$
- $f_{fb} = f_{in}$  (no error)
- $f_{out} = N \times f_{in}$


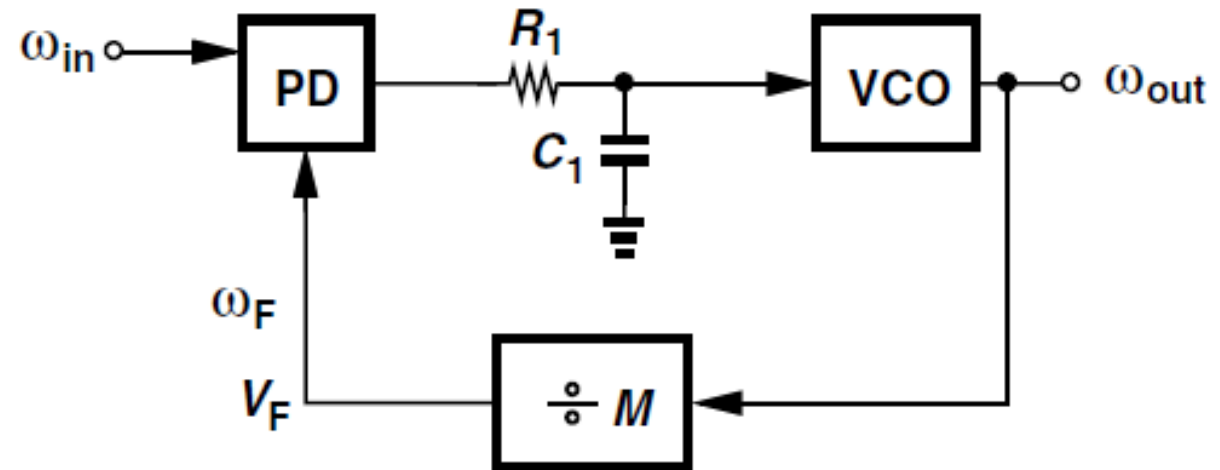 
# Amplifier vs PLL



- ❑ The op-amp circuit amplifies the input voltage by using voltage divider in the FB path
- ❑ The PLL amplifies the frequency by using frequency divider in the FB path
- ❑ The divide ratio  $M$  is called the “modulus”





  
# Voltage-Controlled Oscillator (VCO)

- $V_{out} = A \sin(\phi) = A \sin(\omega t) \rightarrow \omega = \frac{d\phi}{dt} = K_{VCO} V_{ctrl}$   
$$\frac{\phi}{V_{ctrl}} = \frac{K_{VCO}}{s}$$
- Higher frequency means faster phase accumulation


 
# Voltage-Controlled Oscillator (VCO)

$$\square V_{out} = A \sin(\phi) = A \sin(\omega t) \rightarrow \omega = \frac{d\phi}{dt} = K_{VCO} V_{ctrl}$$
$$\frac{\phi}{V_{ctrl}} = \frac{K_{VCO}}{s}$$





# Voltage-Controlled Oscillator (VCO)

□  $\omega_o$ : free running freq       $\omega(t) = K_{VCO}V_{cntl}$ : deviation from  $\omega_o$

$$V_{osc}(t) = E \sin[\omega_o t + \phi(t)]$$

$$\omega_{inst}(t) = \frac{d[\omega_o t + \phi(t)]}{dt} = \omega_o + \frac{d\phi(t)}{dt}$$

$$\omega(t) = \omega_{inst}(t) - \omega_o$$


$$\omega(t) = \frac{d\phi(t)}{dt}$$

$$\phi(t) = \phi(0) + \int_0^t \omega(\tau) d\tau$$

$$\phi(s) = \frac{\omega(s)}{s}$$

$$\omega(t) = K_{osc} V_{cntl}(t)$$

# Frequency Divider

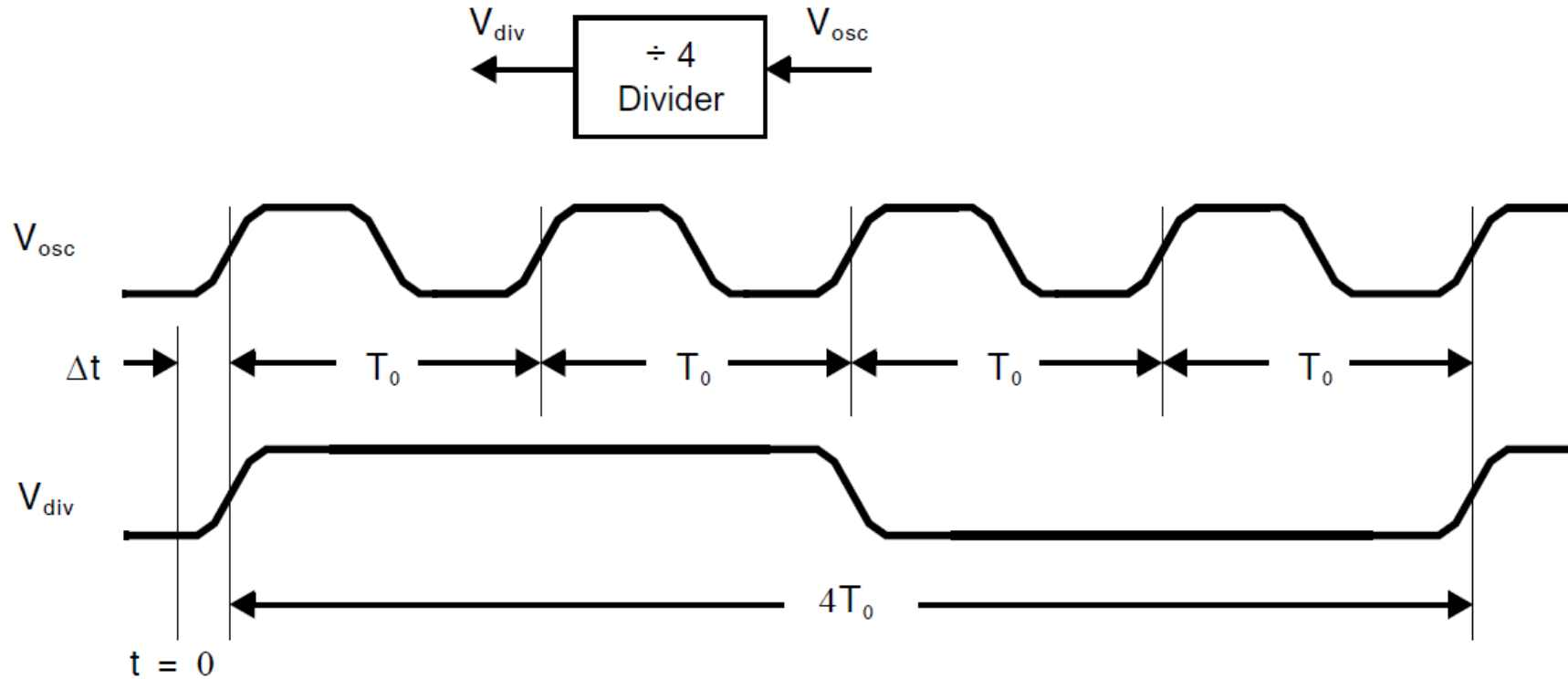


$$\phi = 2\pi \frac{\Delta t}{T_0}$$


$$\phi_{div} = 2\pi \frac{\Delta t}{NT_0} = \frac{\phi}{N}$$

$$\phi_{div}(s) = \frac{\phi(s)}{N}$$


# Ideal Phase Detector

 

# PLL Response to Phase Step

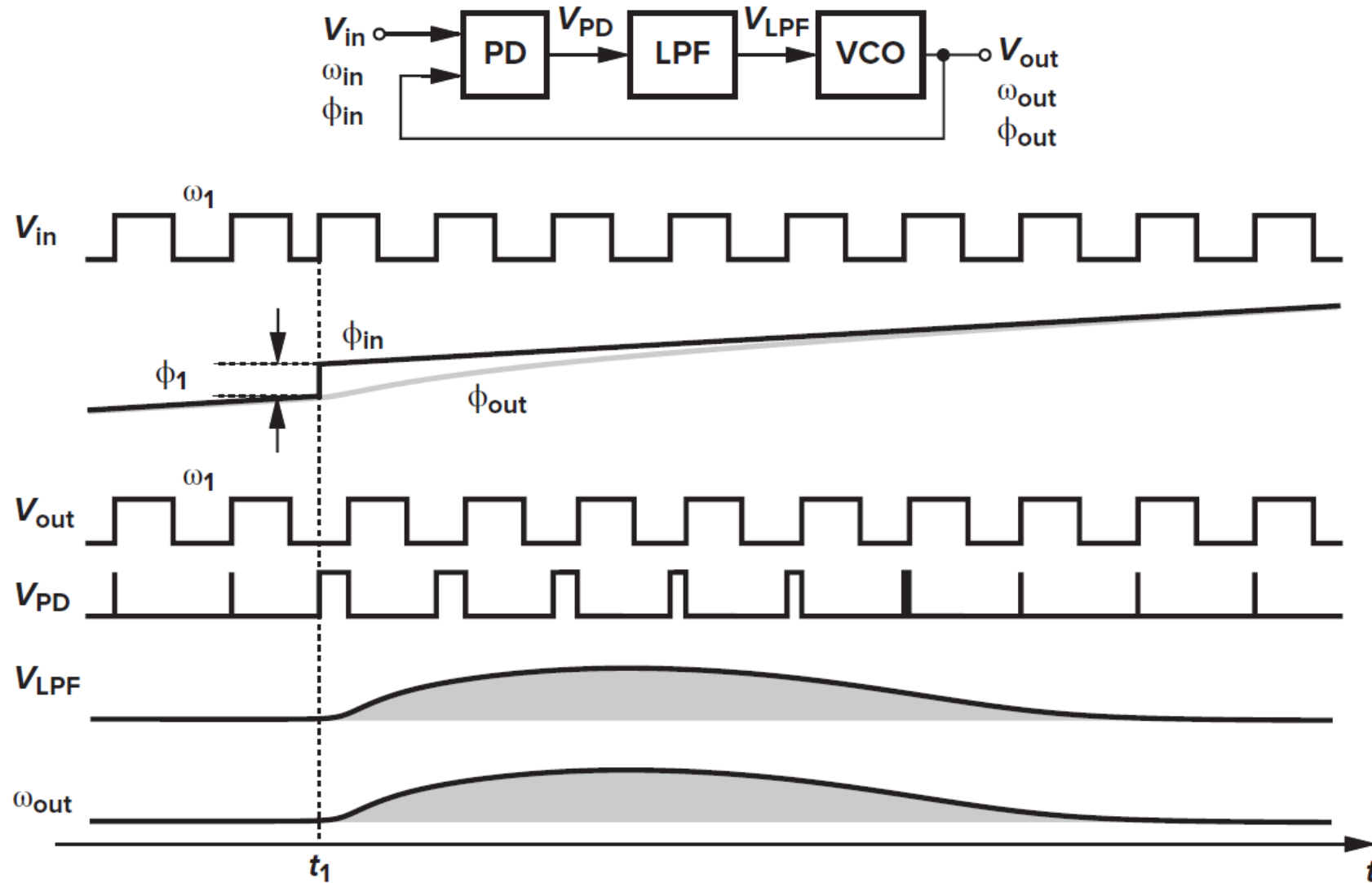


# PLL Response to Frequency Step

 





 
# XOR Phase Detector

- ❑ VCO output and the reference input are both digital signals or have been converted to digital signals by a limiter



     
# XOR Phase Detector

$$\square K_{PD} = \frac{\Delta V_{out}}{\Delta \phi} = \frac{V_0}{\pi}$$


 
# Simple PLL Example

- ❑ The VCO is a negative-Gm LC oscillator tuned by varactors
- ❑ PLL order (no. of poles) = loop filter (LF) order + 1 (VCO)
- ❑ PLL type = no. of ideal integrators (poles at origin)






# Steady State Error

- ❑  $\frac{v_{out}}{v_{in}} = \frac{A}{1+\beta A}$
- ❑  $\frac{v_{err}}{v_{in}} = \frac{1}{1+\beta A} \approx \frac{1}{LG}$
- ❑ Final value theorem:  $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$
- ❑ Steady state error =  $\epsilon_s = v_{err}(t \rightarrow \infty) = \lim_{s \rightarrow 0} \frac{sV_{in}(s)}{LG(s)}$
- ❑ No. of poles at  $s = 0$  (at origin) = no. of ideal integrators
- ❑ How to get zero  $\epsilon_s$ ?
  - Step input:  $V_{in}(s) = \frac{1}{s} \rightarrow$  LG must have one ideal integrator
  - Ramp input:  $V_{in}(s) = \frac{1}{s^2} \rightarrow$  LG must have two ideal integrators
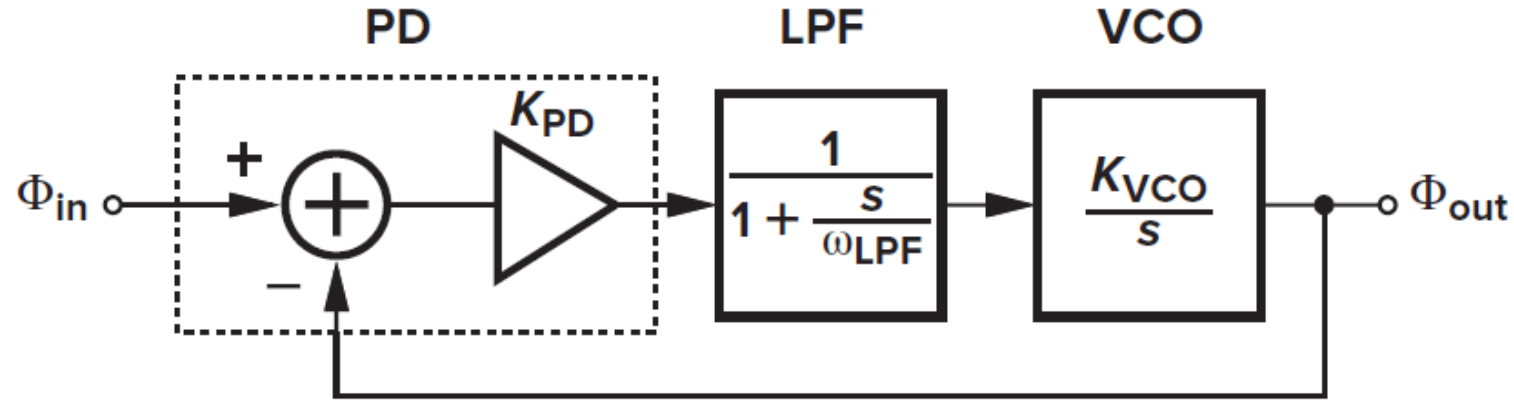
# Type I PLL

- Type I → Loop gain has ONE pole at origin (ONE ideal integrator)



$$\begin{aligned} H(s)|_{open} &= \frac{\Phi_{out}}{\Phi_{in}}(s)|_{open} \\ &= K_{PD} \cdot \frac{1}{1 + \frac{s}{\omega_{LPF}}} \cdot \frac{K_{VCO}}{s} \end{aligned}$$

$$H(s)|_{closed} = \frac{K_{PD}K_{VCO}}{\frac{s^2}{\omega_{LPF}} + s + K_{PD}K_{VCO}}$$

# Type I PLL

- $\Phi_{in} = \int \omega_{in} dt \rightarrow$  the input phase is ramp input
  - Type I has only one integrator  $\rightarrow$  suffer from static phase error
  - Need two ideal integrators for  $\phi_{err} = 0$
  - Two poles at origin  $\rightarrow$  Type II PLL
- Other drawbacks of Type I:
  - Trade-off between  $\omega_{LPF}$  and stability ( $\zeta$ )
  - Limited acquisition range (solved by using PFD)

$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD}K_{VCO}}}$$


$$\omega_n = \sqrt{K_{PD}K_{VCO}\omega_{LPF}}$$





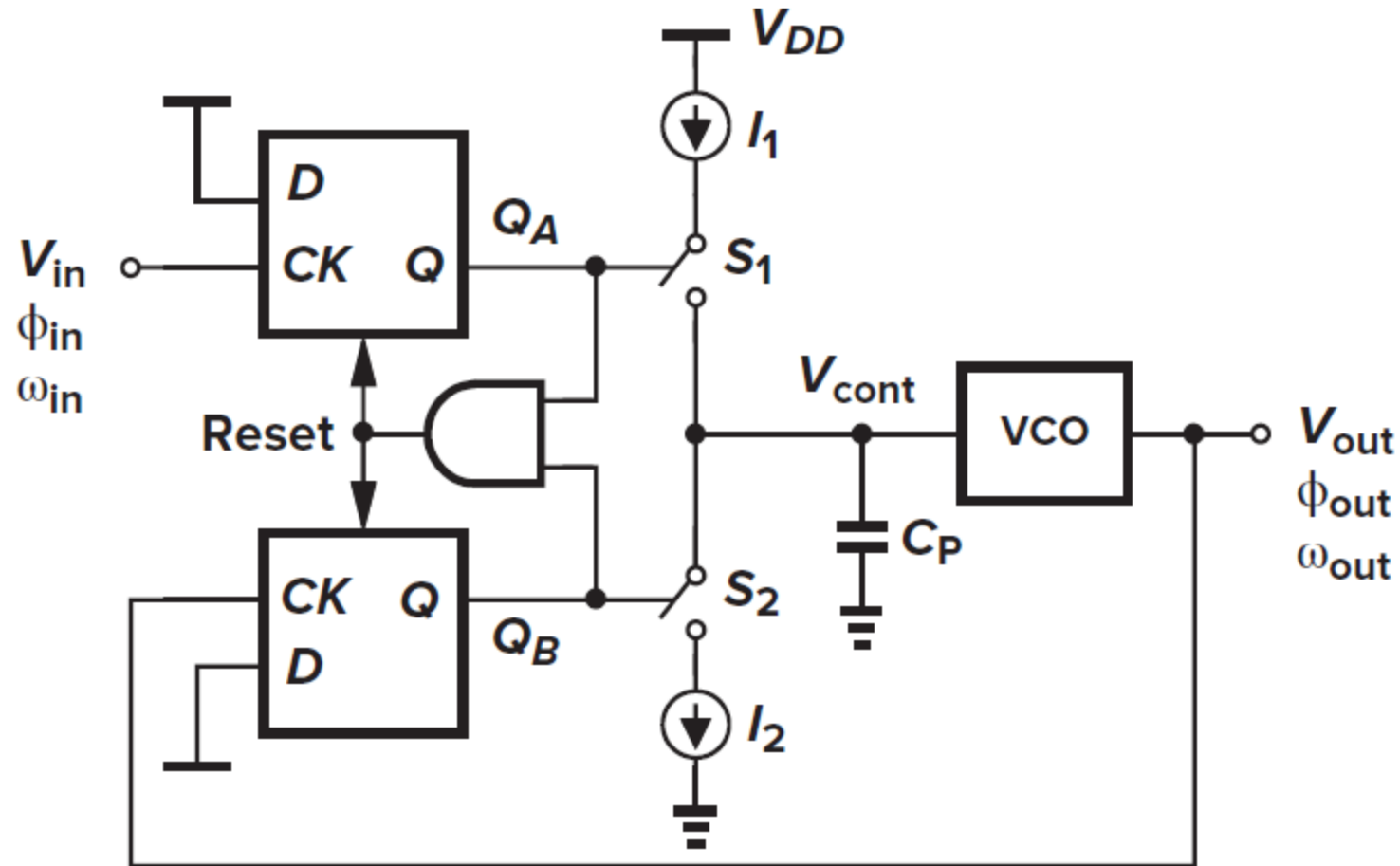
# Type II PLL: Charge Pump (CHP) PLL

- One more ideal integrator in the PD + LF
  - Simply, current source charging a capacitor


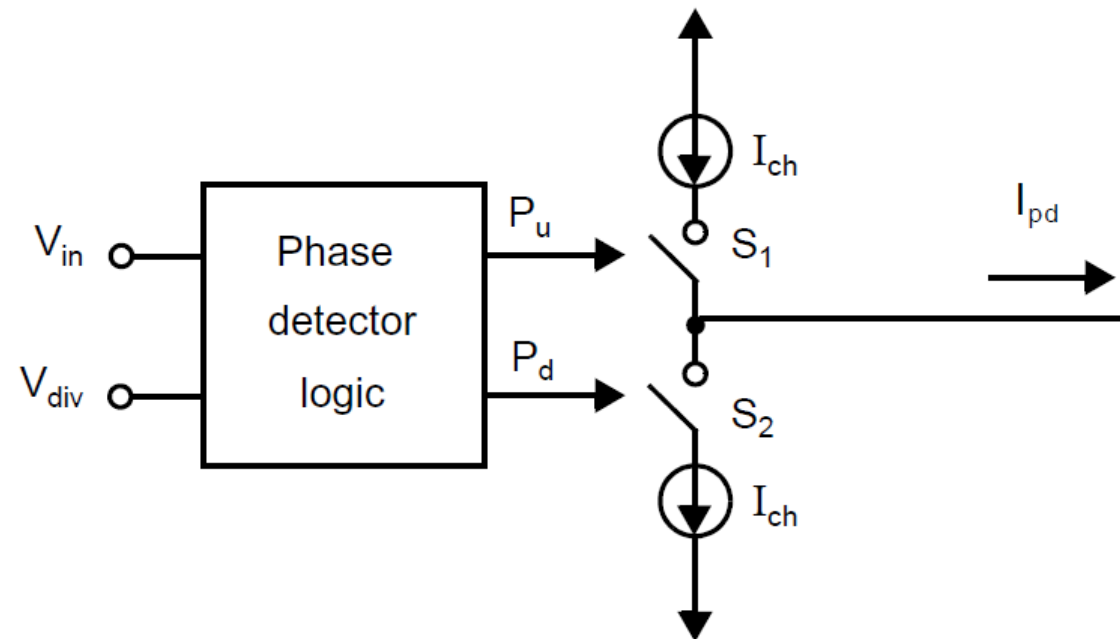
# CHP Phase/Frequency Detector (PFD)


- ❑ Type I has limited acquisition range: because phase detectors produce little information if they sense unequal frequencies
  - Acquisition range can be widened if a frequency detector is added to the loop
- ❑ Three-states:  $P_u = 1$ ,  $P_d = 1$ , and  $P_u = P_d = 0$
- ❑ The falling edges of both  $V_{in}$  and  $V_{div}$  have no effect on  $P_u$  and  $P_d$



# Charge Pump PFD

$$\overline{I_{pd}} = I_{ch} \frac{\phi_d}{2\pi}$$




$$K_{pd} = \frac{I_{ch}}{2\pi}$$

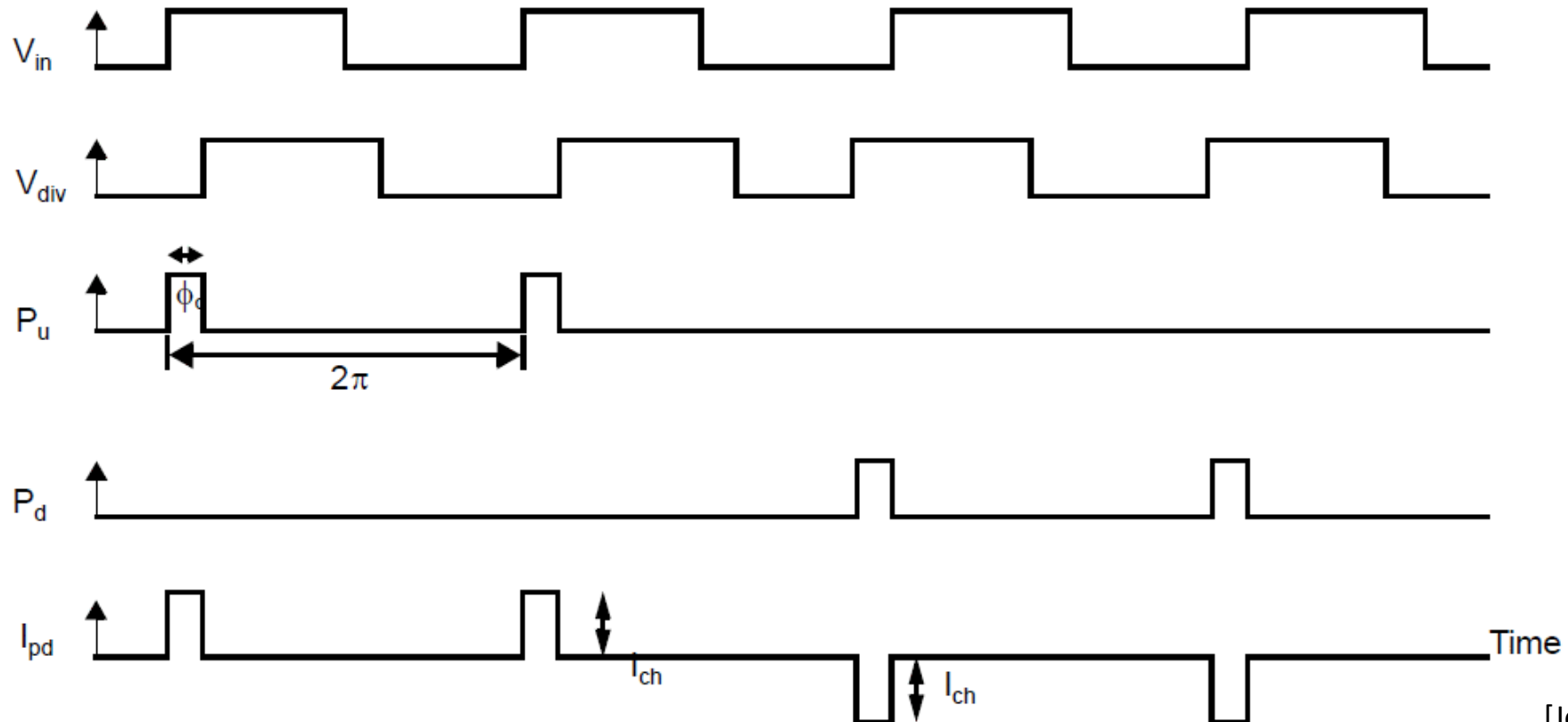





# Charge Pump PFD

- QA: UP
- QB: DOWN (DN)

 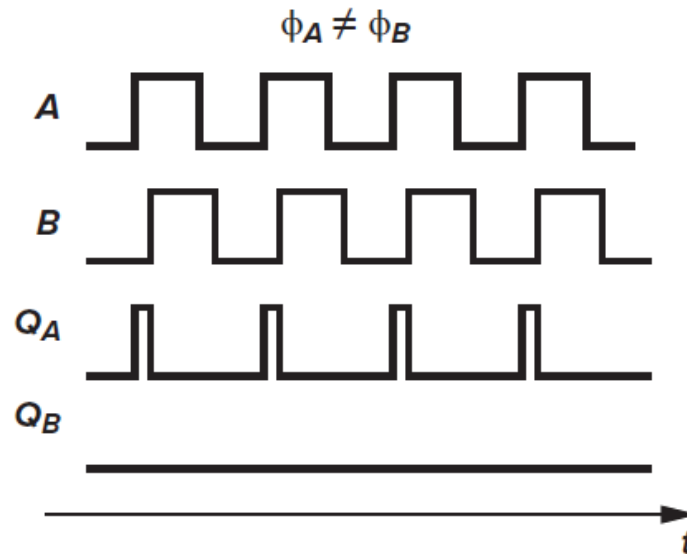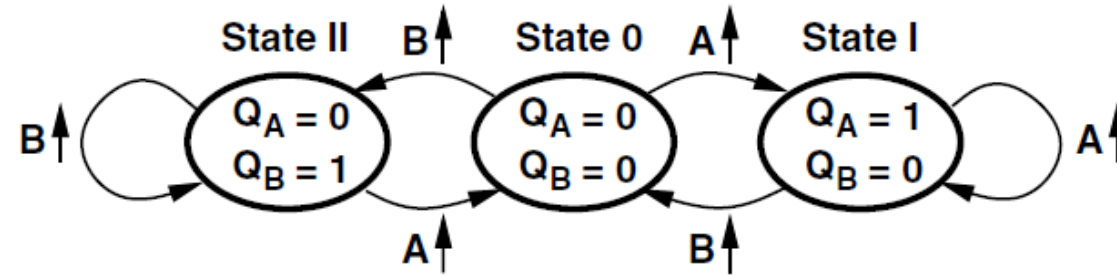

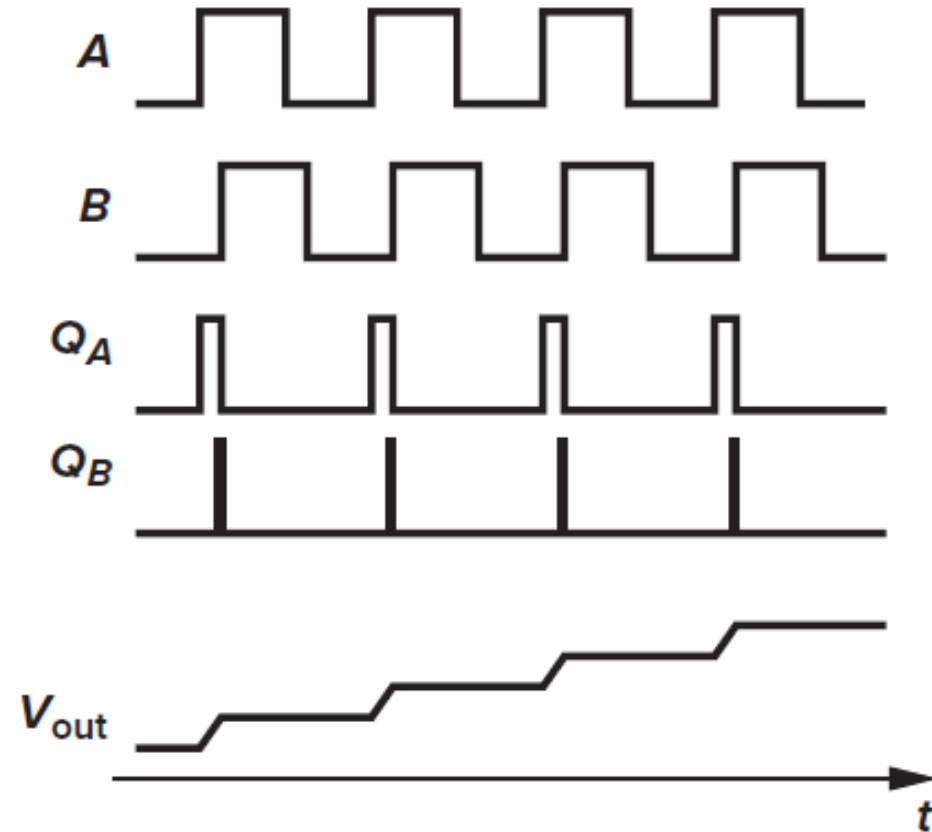
 
# Charge Pump PFD

- A very small input phase error gives growing output
  - Infinite gain  $\rightarrow$  Ideal integrator behavior



 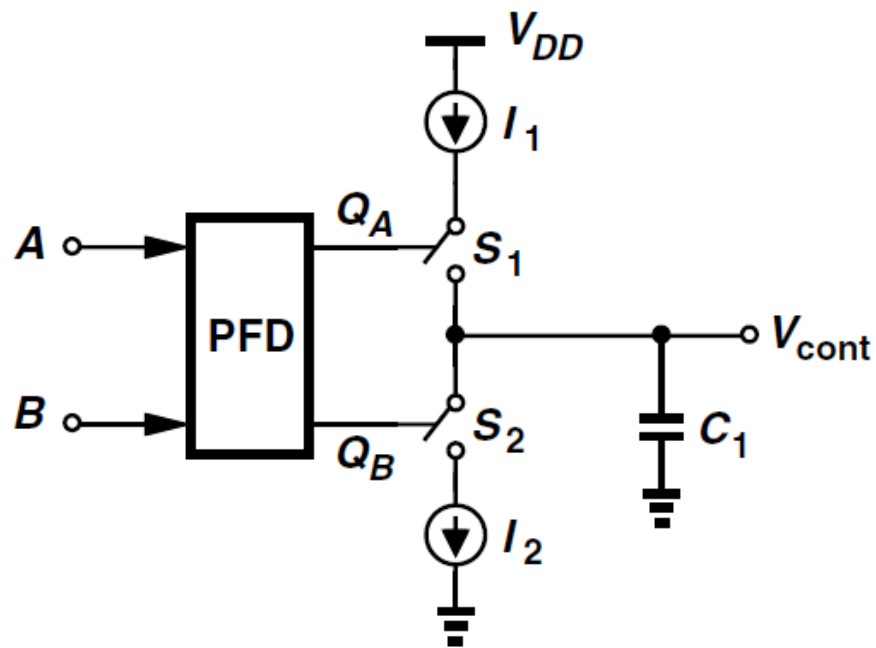
# CHP PFD Continuous-time (CT) Approx

- ❑ CHP PFD is a non-linear system
  - But the waveform can be approximated as a ramp: CT approx


 
# Loop Filter (LF)

- ❑  $R$  introduces a zero necessary for stability
- ❑  $C_2$  introduces a high frequency pole to suppress voltage spikes
  - Current spikes passing through  $R$  will cause voltage spikes
- ❑ Usually  $C_1 \gg C_2$





$$K_{lp} H_{lp}(s) = \frac{V_{ctrl}(s)}{I_{pd}(s)} = \frac{1}{s(C_1 + C_2)} \cdot \frac{1 + sRC_1}{1 + sR\left(\frac{C_1 C_2}{C_1 + C_2}\right)}$$

$$K_{lp} H_{lp}(s) = \frac{V_{ctrl}(s)}{I_{pd}(s)} \cong \frac{1}{C_1} \left( \frac{1 + sRC_1}{s} \right)$$


$$K_{lp} = 1/C_1 \quad \omega_z = 1/(RC_1)$$
 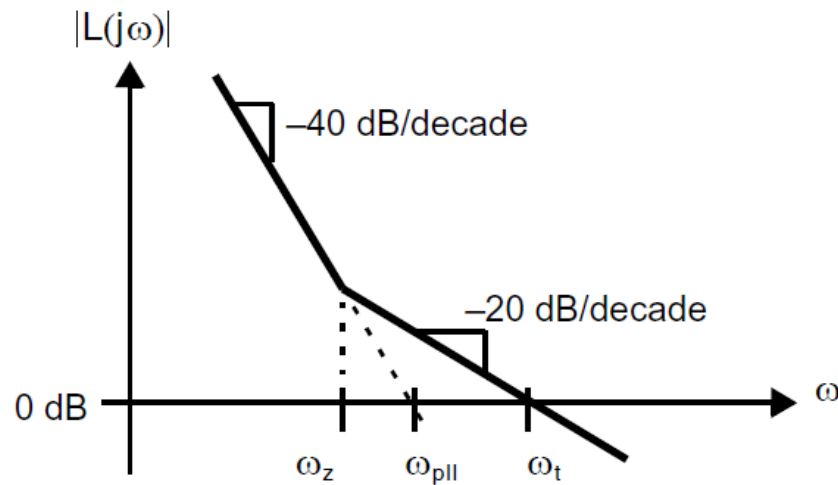
# Bode Plot

- ❑ Two poles at origin
- ❑ The zero is necessary to achieve stability
- ❑ The non-dominant pole due to  $C_2$  reduces the PM
  - But necessary to filter out voltage spikes



# Linearized Small-Signal Model

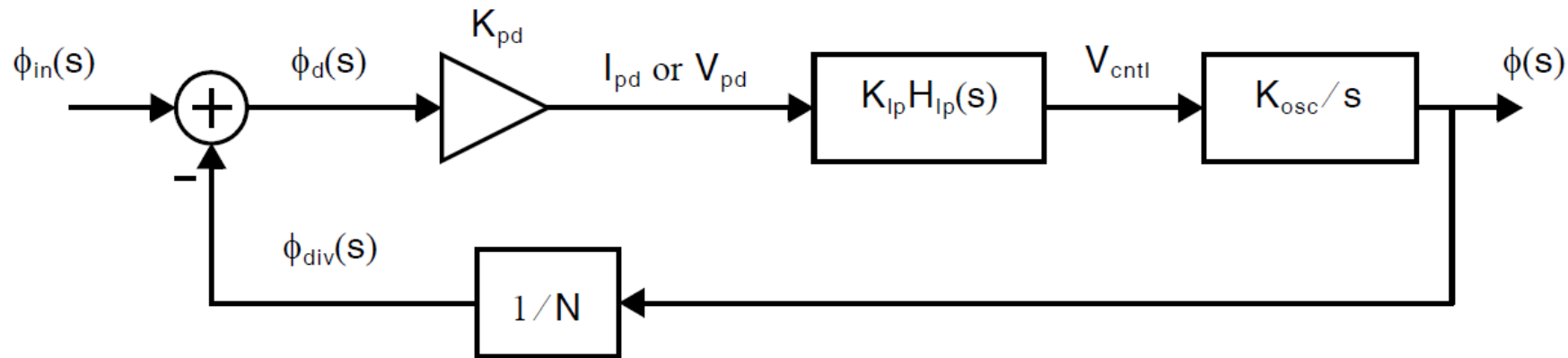

$$\frac{\phi_d(s)}{\phi_{in}(s)} = \frac{1}{1 + L(s)}$$

$$L(s) = \frac{K_{pd} K_{lp} K_{osc} H_{lp}(s)}{Ns}$$

$$\frac{\phi_d(s)}{\phi_{in}(s)} = \frac{s}{s + K_{pd} K_{lp} K_{osc} H_{lp}(s)/N}$$

# PLL Model

□ Loop constant (loop resonance frequency)

$$\omega_{\text{pll}} = \sqrt{\frac{K_{\text{pd}}K_{\text{lp}}K_{\text{osc}}}{N}}$$

□ Loop gain

$$L(s) = \frac{\omega_{\text{pll}}^2}{s^2} \cdot \left(1 + \frac{s}{\omega_z}\right)$$

□ Error TF

$$\frac{\phi_d(s)}{\phi_{\text{in}}(s)} = \frac{1}{\omega_{\text{pll}}^2} \cdot \frac{s^2}{\left(1 + \frac{s}{\omega_z} + \frac{s^2}{\omega_{\text{pll}}^2}\right)}$$

□ Phase TF

$$H(s) = \frac{\phi(s)}{\phi_{\text{in}}(s)} = \frac{N(1 + s/\omega_z)}{1 + \frac{s}{\omega_z} + \frac{s^2}{\omega_{\text{pll}}^2}}$$



# Closed Loop Response

$$H(s) = \frac{\phi(s)}{\phi_{in}(s)} = \frac{N(1 + s/\omega_z)}{1 + \frac{s}{\omega_z} + \frac{s^2}{\omega_{pll}^2}}$$

$$\omega_{pll} = \sqrt{\frac{K_{pd}K_{lp}K_{osc}}{N}}$$

$$Q = \frac{\omega_z}{\omega_{pll}}$$

$$\zeta = 1/2Q$$

  



# Q = 0.5

- ❑ An all-pole system with  $Q = 0.5$  will have no overshoot or peaking
  - But the PLL has a zero which introduces both slight overshoot and peaking (jitter peaking) even when  $Q = 0.5$
- ❑  $Q = 0.5$  gives reasonable LF time constant  $\rightarrow$  can be implemented on-chip

$$\omega_z = \omega_{\text{pll}}/2$$

$$H(s) = \frac{N(1 + s/\omega_z)}{(1 + s/\omega_{\text{pll}})^2}$$

$$\omega_{3\text{dB}} = 2.5\omega_{\text{pll}}$$

- ❑  $Q = 0.1$  offers even better tracking behavior, but generally demands a larger loop-filter time constant for the same loop bandwidth

# Resolution-Bandwidth Trade-off

□ For integer-N PLL, the tuning resolution is determined by  $\omega_{in}$

- The smaller  $\omega_{in}$ , the finer the resolution
- If finer resolution is required, use fractional-N PLL

□ PLL is a discrete time system


- $\omega_{in}$  is the sampling frequency
- For the PLL CT linear model approximation to be valid

$$\omega_{3dB} \ll \omega_{in}$$
$$\omega_{3dB} < 0.1\omega_{in}$$

- Moreover, we need  $\omega_{3dB} \ll \omega_{in}$  to filter out the reference spurs (reference transients modulate the VCO)
- The smaller  $\omega_{in}$ , the slower the loop (longer settling time)
- Also higher loop bandwidths permit the use of smaller components in the loop filter
 
# Jitter

- ❑ Jitter is the random variation in clock transition instants



# Phase Noise


- Phase noise is the frequency-domain representation of jitter

- Jitter ( $\tau_k$ ) to phase noise ( $\phi_k$ ):

$$t_k = kT_o + \tau_k \qquad \phi_k = \tau_k \cdot \frac{2\pi}{T_o}$$


- A pure sinusoid will have a single tone at  $1/T_o$

 - A practical signal will have power in a range of frequencies around the pure tone (the carrier)



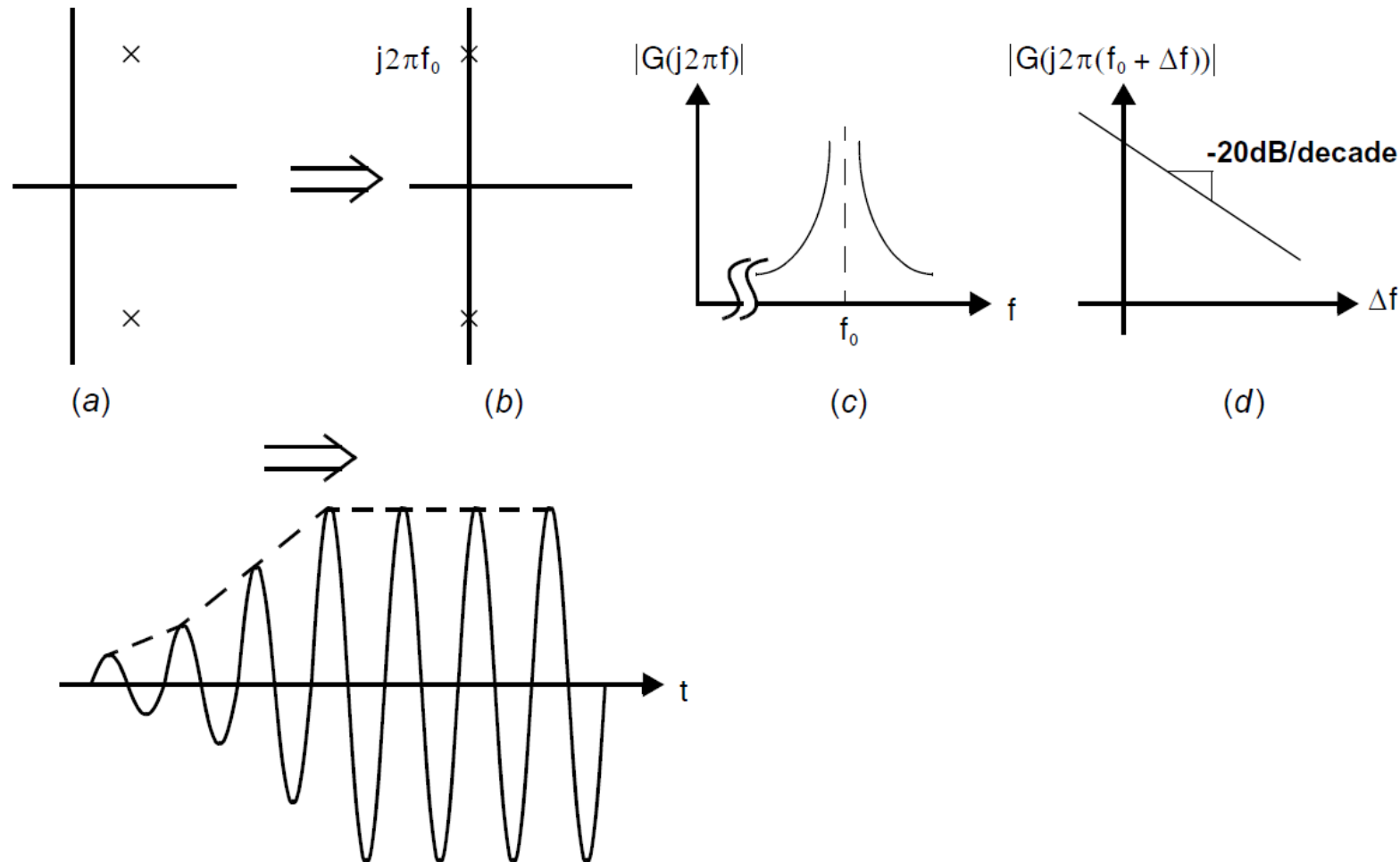
# Oscillator Response

- ❑ The oscillator has a pole at  $f_o$
- ❑ Away from the pole the magnitude decays at -20dB/decade


 
# Oscillator Phase Noise

- ❑ 1<sup>st</sup> component: White noise not filtered by the oscillator (e.g., buffer noise)
- ❑ 2<sup>nd</sup> component: White noise up-converted and shaped by the oscillator response
- ❑ 3<sup>rd</sup> component: Flicker noise up-converted and shaped by the oscillator response



# PLL Noise Sources

- ❑ Input and divider phase noise are filtered by the PLL transfer function (LPF) (output follows input within loop bandwidth)


$$H(s) = \frac{K_{pd}K_{lp}K_{osc}H_{lp}(s)/s}{1 + L(s)}$$

- ❑ VCO phase noise sees a HPF (attenuated within loop bandwidth)

$$H_{osc}(s) = \frac{1}{1 + L(s)}$$


- ❑ Loop filter phase noise sees a BPF

$$H_n(s) = \frac{K_{osc}/s}{1 + L(s)}$$

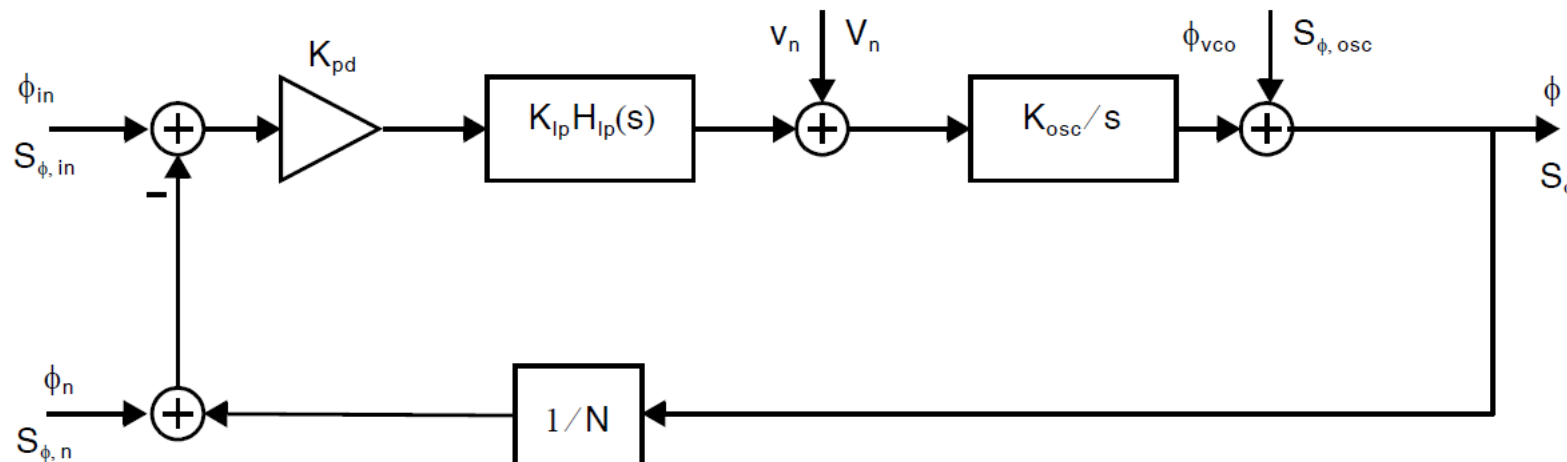
 
# PLL Noise Sources


- ❑ The PLL loop bandwidth sets the cutoff frequency below which VCO phase noise is attenuated and above which input reference (and divider) phase noise is attenuated
- ❑ Solve Razavi RF Example 9.26 and 9.27




 
# PLL Output Noise

- ❑ The example below ignores VCO white noise component ( $h_0 = 0$ )
- ❑ Assuming a high-quality (low-noise) reference
  - PLL loop bandwidth should be maximized to minimize the contribution of VCO phase noise to the PLL's output jitter



---

**Thank you!**

# Assignments

---

- ❑ Read “pll\_design.pdf”
  - Part of my MSc thesis (2010)