
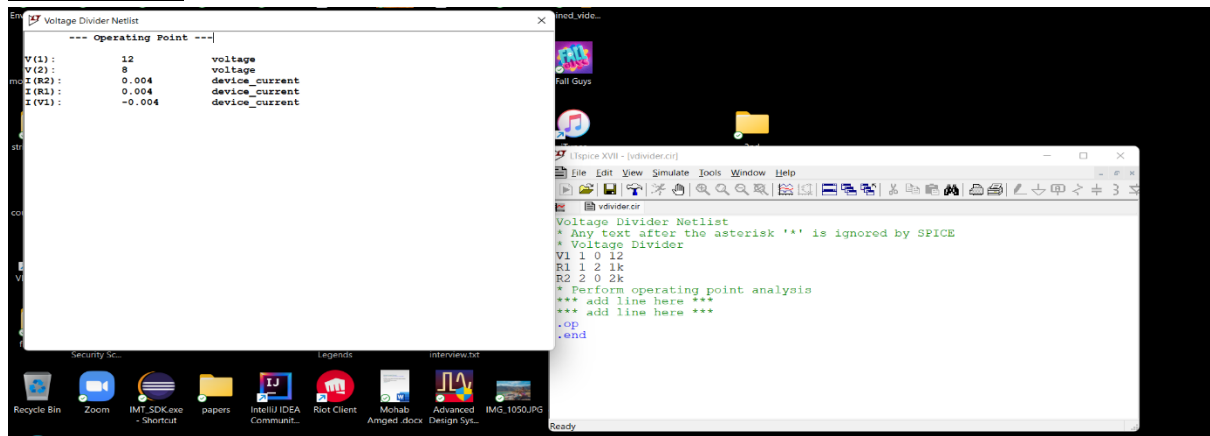


Part 1 :


Question 1:

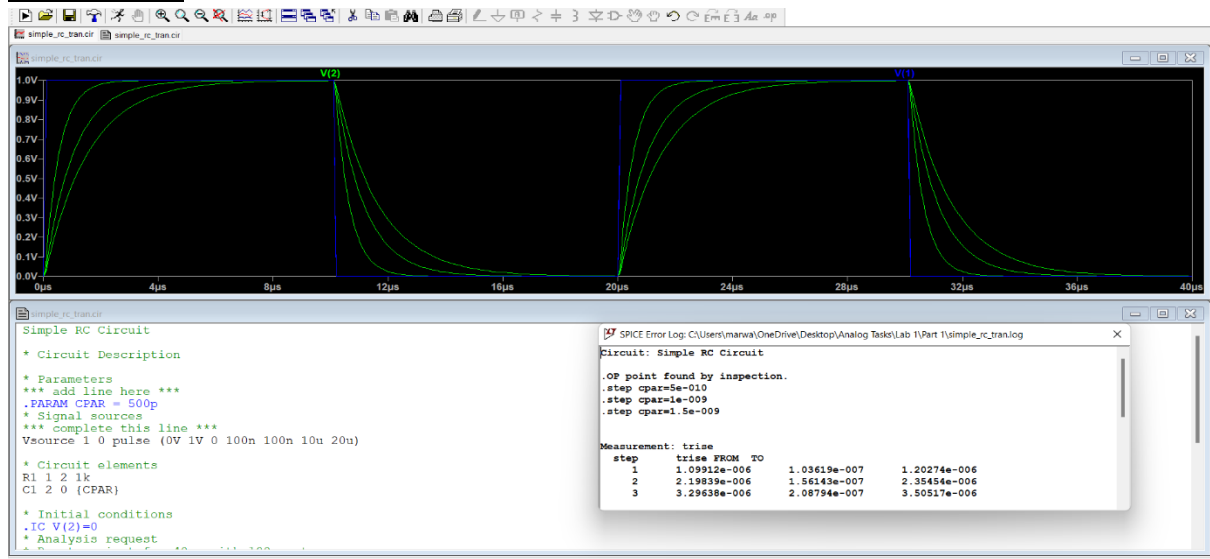

Question 2:



Question 3:

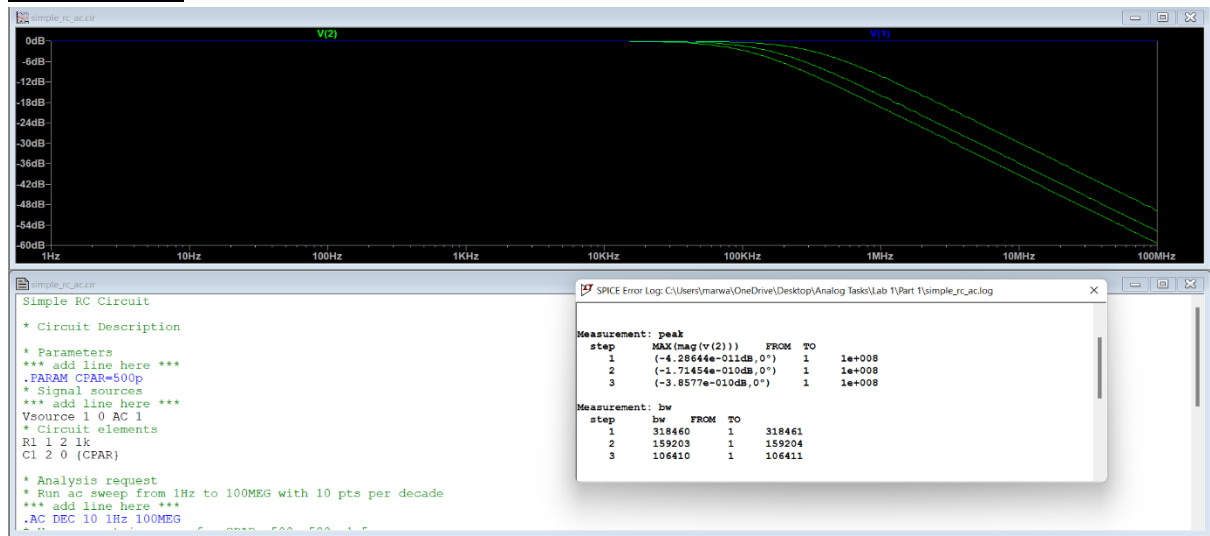

Part 2 :

Question 1 :

From the given data op-amp open loop gain will be 10000(gmR) and UGF 10 MEGAhz

Therefore a pole at 1Khz($RC=1/\omega$) so we have two equations to get R,C,gm.

We no other constrains on the circuit elements so we can make an assumption for one element of the circuit, so let $R=1k$, from the equations $gm=10$, $C=159.155n$.

Op-amp sub Circuit Netlist:

//////There is a Typo error in one of the comments I meant Voltage Controlled Current Source not Current Controlled Voltage Source of This Pic.//////

```
.SUBCKT opamp 1 2 3
* Connections //
* //
* // Vin-
* // Vin+
* //
* output node

* First Stage of the op amp
* Differential Inputs
* +Ve Terminal Open Current Source (Topology Requirement to have atleast 2 connections to a node )
Iopen 2 0 0A
* -Ve Terminal Open Current Source (Topology Requirement to have atleast 2 connections to a node )
Iopen1 3 0 0A

* Define the Current controlled Voltage source controlled by the Differential inputs
Gin 0 4 2 3 10


* Defining The Passive elements to get the required specs 10000 Gain and ugf 10 MHz
R1 4 0 1k
*G*R1=10000
C1 4 0 159.155n
* R*C = 1.59155E-4
* G*R=1+jwRC @ UGF

* First stage Completed

* 2nd Stage of the op amp
* Ideal Output Buffer
* Define The Voltage Controlled Voltage Source with output equal to the voltage across the Rc Components
Eout 1 0 4 0 1

.ends opamp
```


Op-Amp Sub Circuit Bode Plot: UGF=10Megahz , DC_Gain=80db → 10000

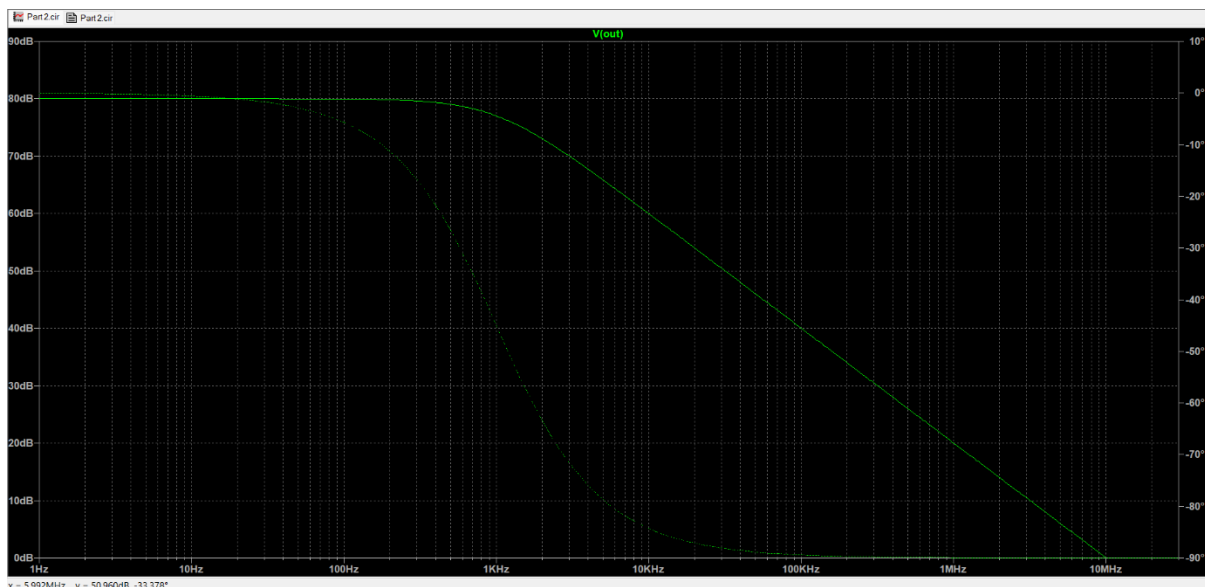

Question 2 :


Non-Inverting Amp TF analysis using 1V DC :

Gain almost 10

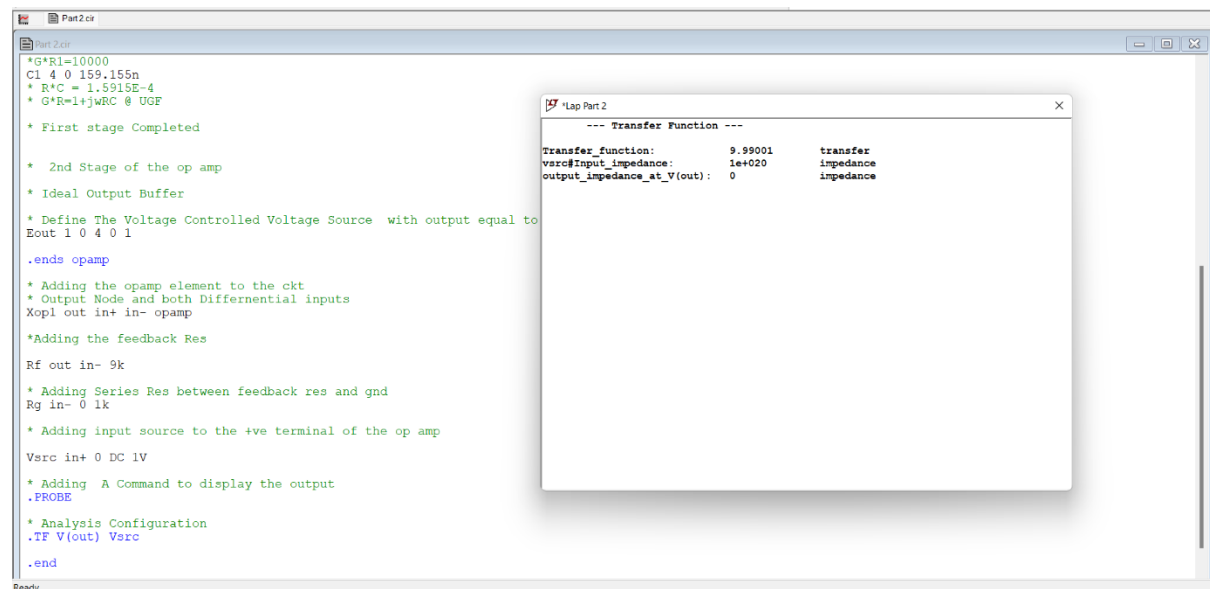

Question 3 :

Transient Analysis using sine wave for 2 complete cycles of the input with Amp 1v and 1khz freq , Peak Values of Vsig and Vout found using measure command.

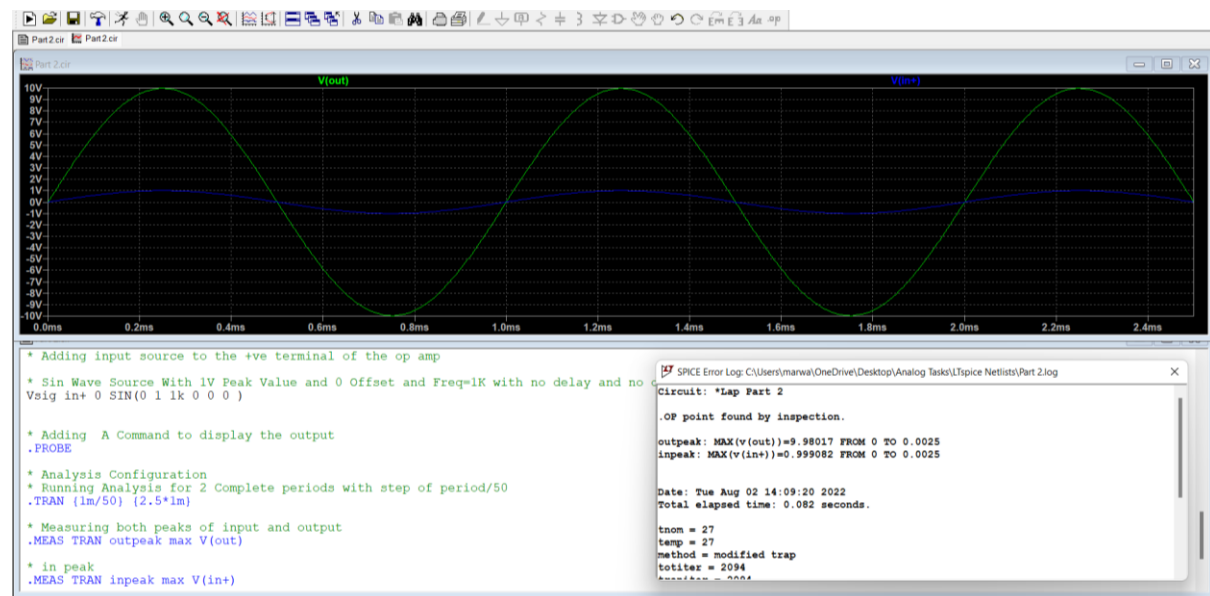

Question 4 :

The Voltage gain is 10

Hand Analysis	TF Analysis	Transient Analysis
$A=1+(R_F/R)=1+9/1=10$	$A=9.99001$	$A=\text{Output Peak}/\text{Input Peak}$ $A=9.98017/0.999082=9.989340214$


Hand Analysis is the ideal value of the gain , Transfer function and transient analysis is almost the same but the slight difference might be due to the solving of the differential equations at the transient analysis while solving easier model at the TF analysis.

(Both TF And Transient analysis are Accurate)

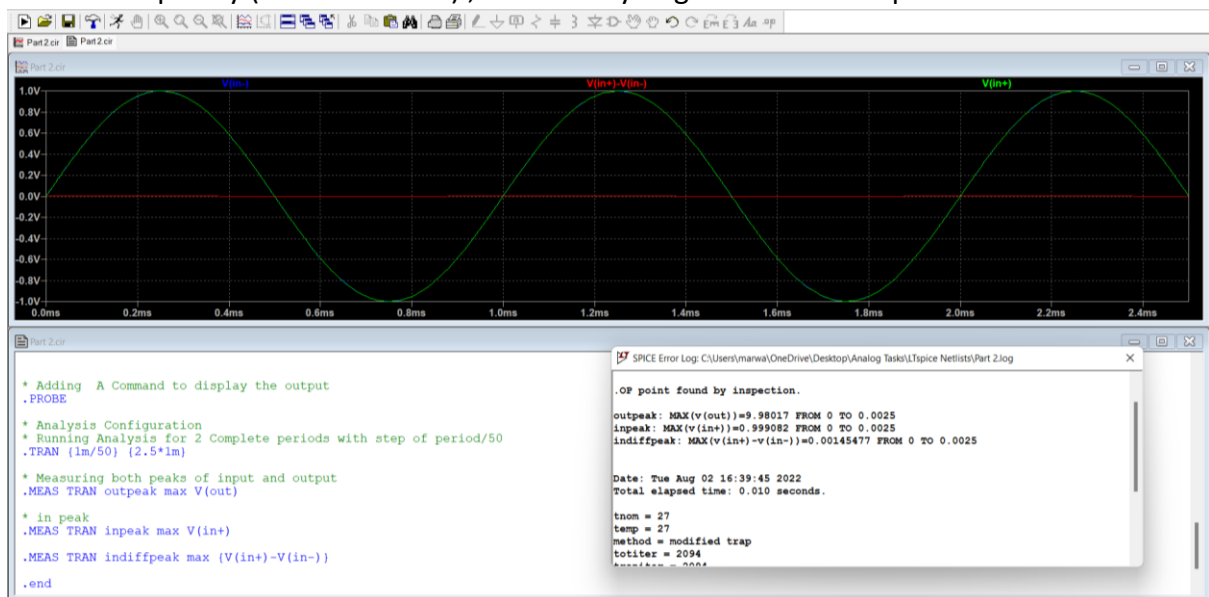
Question 5 :

The Differential Input signal is the red signal amplitude Ideally is equal to 0 as V_{in+} Ideally equal to V_{in-} due to the Very Large Gain and the -Ve feedback stables the system, See hand analysis.

At 1khz frequency (Within the BW) , Gain is very large Differential Input=0 :



Hand Analysis :

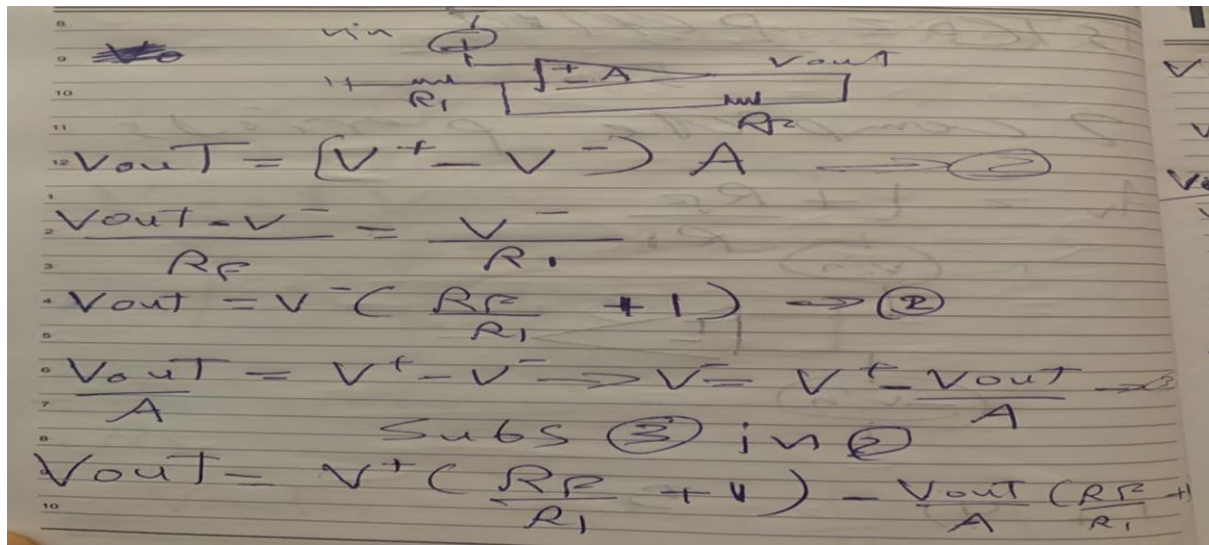

Handwritten circuit diagram and equations for a differential amplifier:

Circuit diagram: A differential amplifier with input voltage V_{in} applied to the non-inverting input of the first op-amp. The feedback resistor is R_F and the input resistor is R_1 . The output is V_{out} .

Equations:

$$V_{out} = (V^+ - V^-) A \quad \text{--- (1)}$$


$$\frac{V_{out}}{R_F} = \frac{V^-}{R_1} \quad \text{--- (2)}$$

$$V_{out} = V^- \left(\frac{R_F}{R_1} + 1 \right) \quad \text{--- (3)}$$

$$\frac{V_{out}}{A} = V^+ - V^- \Rightarrow V^- = V^+ - \frac{V_{out}}{A} \quad \text{--- (4)}$$

Subs (4) in (3)
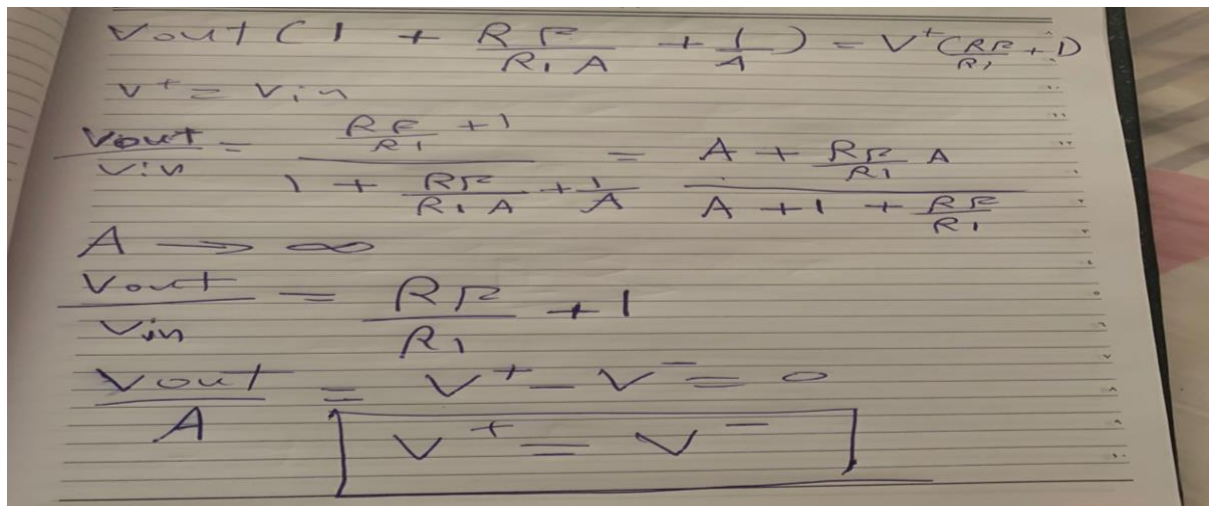
$$V_{out} = V^+ \left(\frac{R_F}{R_1} + 1 \right) - \frac{V_{out}}{A} \left(\frac{R_F}{R_1} + 1 \right)$$



Handwritten equations for the differential amplifier:

$$V_{out} \left(1 + \frac{R_F}{R_1 A} + \frac{1}{A} \right) = V^+ \left(\frac{R_F}{R_1} + 1 \right)$$

$$V^+ = V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{R_F}{R_1} + 1}{1 + \frac{R_F}{R_1 A} + \frac{1}{A}} = \frac{A + \frac{R_F}{R_1} A}{A + 1 + \frac{R_F}{R_1}}$$

$$A \rightarrow \infty$$


$$\frac{V_{out}}{V_{in}} = \frac{R_F}{R_1} + 1$$

$$\frac{V_{out}}{A} = V^+ - V^- = 0$$

$$V^+ = V^-$$

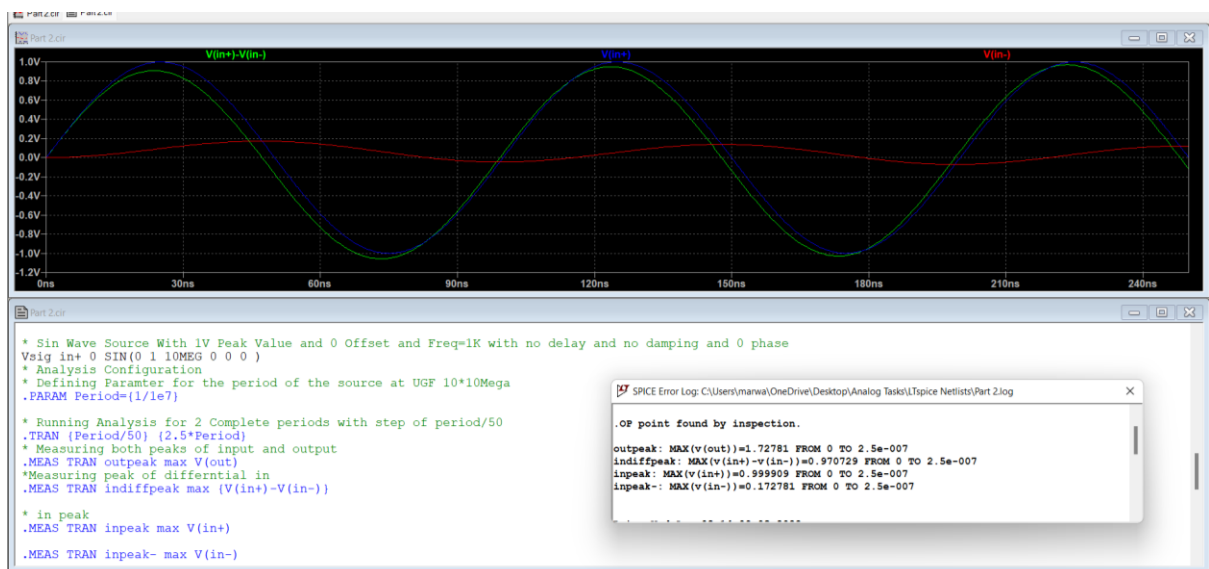Question 6:

At 10Megahz (UGF) Gain magnitude is Equal to 1 :



Comment:

V_{in+} not equal to the V_{in-} as in the very large gain case ,


$V_{in-} = 1/10 * V_{out}$, Simulation Results are equal to the Hand analysis results.

Question 7:

Dc Gain and Bandwidth and UGF (GBW) Calculated using measure and visible in the figure ,
UGF Clear In the drawing 10 Megahz @ 0db $\rightarrow V_{in} = V_{out}, \text{Gain} = 1$.

14 db Gain for the 4k Resistor.

20 db Gain for the 9k Resistor.

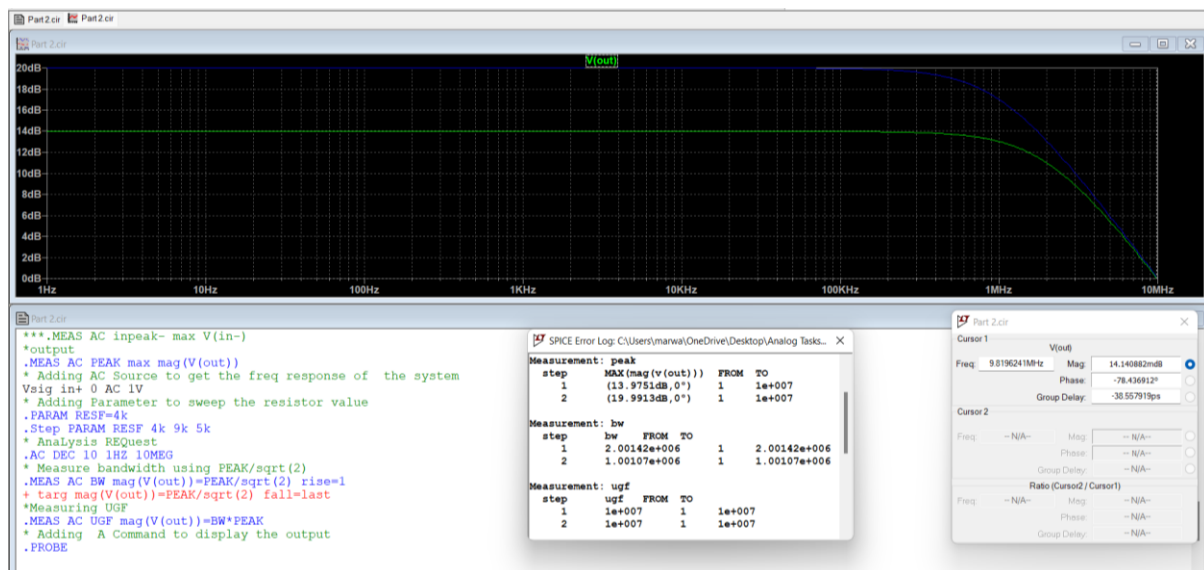

Question 8:

No there will be no clipping , The Amplifier Amplifies the signal within The Bandwidth regarding its magnitude.

Question 9:

Comment:

The Results are almost the same from Hand Analysis and Ac Analysis (Ac Analysis is very accurate).

See Table below:

Type	Hand Analysis	AC Analysis
Gain	<u>For 4K Resistor :</u> Gain =5 , 14db <u>For 9K Resistor :</u> Gain =10 , 20db	<u>For 4K Resistor :</u> Gain =4.9975, 13.9751db <u>For 9K Resistor :</u> Gain =9.9899 , 19.9913db
Cut off Frequency	<u>For 4K Resistor :</u> $F_c = 2\text{Mhz}$ <u>For 9K Resistor :</u> $F_c = 1\text{Mhz}$	<u>For 4K Resistor :</u> $F_c = 2.00142\text{Mhz}$ <u>For 9K Resistor :</u> $F_c = 1.00107\text{Mhz}$
GBW(UGF)	<u>For 4K Resistor :</u> GBW=10Mhz <u>For 9K Resistor :</u> GBW= 10Mhz	<u>For 4K Resistor :</u> GBW=10.00209645Mhz <u>For 9K Resistor :</u> GBW= 10.00058919Mhz