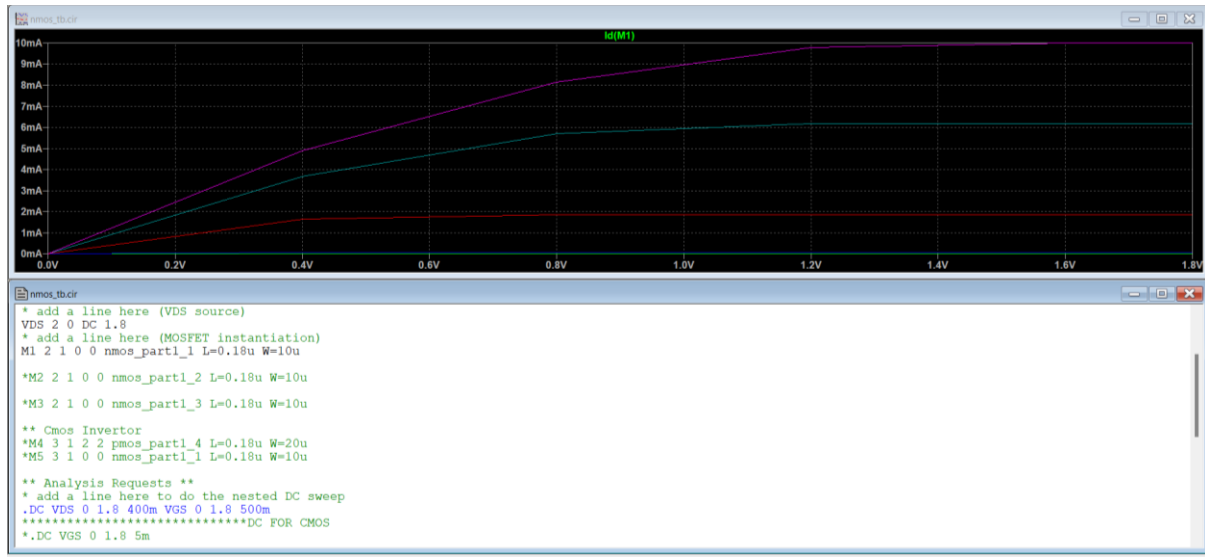


PART1:

Question 1:


ID Vs VDS with different vgs .(DC SWEEP)



Nmos Model Used :


```
*-----*
* Part 1.1
.MODEL nmos_part1_1 NMOS [LEVEL=1 KP=183.67u VTO=0.4]
*-----*
```

The Spice Error log Doesn't recommend using Level 1 Model With This length it may be not Accurate (due to Short Channel Effect),

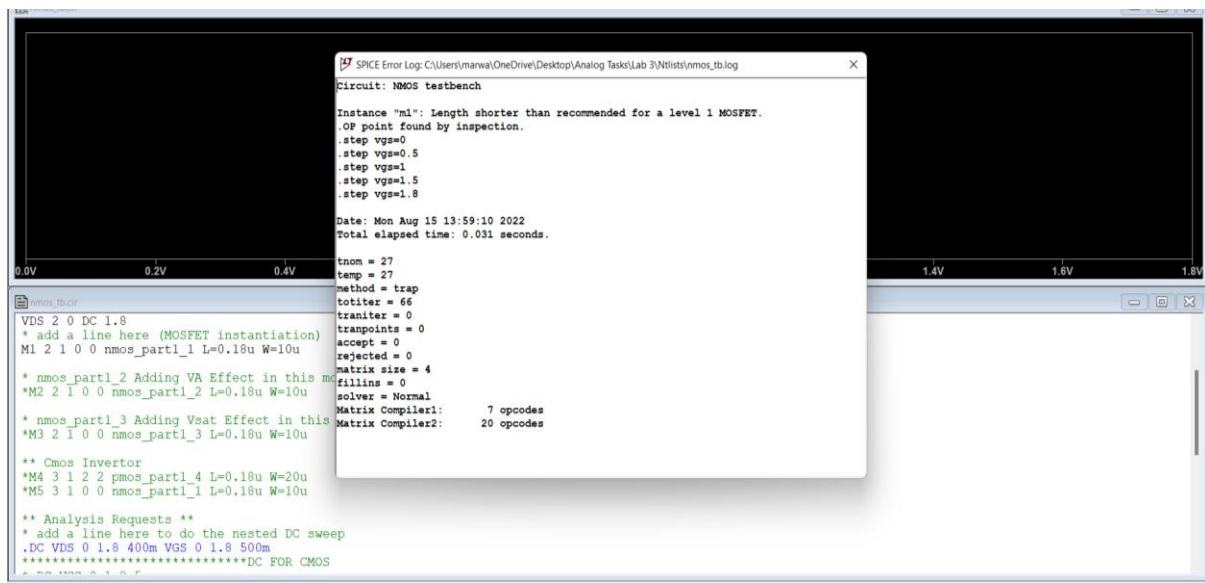

 Question 2:

Added Early Effect (Ro Effect) you can See slope at the saturation region .




Model Used :

```
* Part1.2
* add a line here (same as Part 1.1 except for one more parameter)
* Don't forget to change the model name to nmos_part1_2
.MODEL nmos_part1_2 NMOS [LEVEL=1 KP=1.8367e-4 VTO=0.4 LAMBDA=0.1 ]
```

Question 3:

Velocity Saturation Effect Added.

 


Model Used :

```
* Part 1.3
*.add a line here (same as Part 1.2 except for one more parameter)
.MODEL nmos_part1_3 NMOS [LEVEL=2 KP=1.8367e-4 VTO=0.4 LAMBDA=0.1 VMAX=3.34e5 ]
*-----*
```

Question 4:

Vth must be -ve value (Pmos).

Cmos Invertor Dc Characteristics

 

Cmos Invertor Netlists

```
cmos_inv_dcir
CMOS inverter DC sweep

** Circuit Description **
* power supply
VDS 2 0 DC 1.8
*add a line here

* input
VIN 1 0 DC 0V
* circuit

*add two lines here (NMOS and PMOS instantiation)
** CMOS Inverter
M4 3 1 2 2 pmos_part1_4 L=0.18u W=20u
M5 3 1 0 0 nmos_part1_1 L=0.18u W=10u

*add a line here include the model file
* Including Libs
.INC my_nmos.lib
.INC my_pmos.lib
** Analysis Requests **
.DC VIN 0 1.8 0.05

** Outputs Requests **
.PROBE

.END
```

Pmos Library :

```
*Pmos Lib Question 1
* Part 1.4
.MODEL pmos_part1_4 PMOS [LEVEL=1 KP=91.835u VTO=-0.4 ]
*-----*

* Adding Cj and CJSW Effects
* Part 1.6
.MODEL pmos_part1_6 PMOS [LEVEL=1 KP=91.835u VTO=-0.4 LAMBDA=0.1 CJ=1m CJSW=100p]
*-----*
```

Nmos Library :

```
*-----*
* Part 1.1
.MODEL nmos_part1_1 NMOS [LEVEL=1 KP=183.67u VTO=0.4]
*-----*

* Part1.2
* add a line here (same as Part 1.1 except for one more parameter)
* Don't forget to change the model name to nmos_part1_2
.MODEL nmos_part1_2 NMOS [LEVEL=1 KP=1.8367e-4 VTO=0.4 LAMBDA=0.1 ]
*-----*

* Part 1.3
*.add a line here (same as Part 1.2 except for one more parameter)
.MODEL nmos_part1_3 NMOS [LEVEL=2 KP=1.8367e-4 VTO=0.4 LAMBDA=0.1 VMAX=3.34e5 ]
*-----*

* Part 1.6
* add a line here (same as Part 1.3 but you have to add CJ and CJSW. Take care of the units)
.MODEL nmos_part1_6 NMOS [LEVEL=1 KP=1.8367e-4 VTO=0.4 LAMBDA=0.1 CJ=1m CJSW=100p]
```

Question 5:

Transient Graph :



Netlist:

```
CMOS inverter tran analysis

* add a line here include the model file
.INC my_nmos.lib
.INC my_pmos.lib

** Circuit Description **

VDD 2 0 DC 1.8V

* add a line here (pulse source)
Vtran 1 0 PULSE (0 1.8 0 5p 5p 50p 100p)
* add two lines here (NMOS and PMOS instantiation )
** Cmos Inverter
M4 3 1 2 2 pmos_part1_4 L=0.18u W=20u
M5 3 1 0 0 nmos_part1_1 L=0.18u W=10u
** Analysis Requests **
*add a line here (use transient analysis for two periods)
.TRAN 5p 200p

*Measuring Delay
.MEAS TRAN TRISE
+ TRIG when v(3) = 0.1 CROSS = 1
+ Targ when v(3) = 0.9 CROSS = 1
.END
```

Delay Measurement:

```
SPICE Error Log: C:\Users\marwa\OneDrive\Desktop\Analog Tasks\Lab 3\Ntlists\cmos_inv_tran.log
Circuit: CMOS inverter tran analysis

Instance "m5": Length shorter than recommended for a level 1 MOSFET.
Instance "m4": Length shorter than recommended for a level 1 MOSFET.
Direct Newton iteration for .op point succeeded.
Heightened Def Con from 2.5e-012 to 2.50305e-012
Heightened Def Con from 5.75e-011 to 5.75004e-011
Heightened Def Con from 1.025e-010 to 1.02524e-010
Heightened Def Con from 1.575e-010 to 1.575e-010


trise=-4.59381e-013 FROM 2.96185e-012 TO 2.50247e-012

Date: Mon Aug 15 14:19:08 2022
Total elapsed time: 0.127 seconds.

tnom = 27
temp = 27
method = modified trap
totiter = 3355
traniter = 3348
tranpoints = 1257
accept = 1171
rejected = 90
matrix size = 5
fillins = 0
solver = Normal
Matrix Compiler1: 132 bytes object code size 0.1/0.1/[0.0]
Matrix Compiler2: 335 bytes object code size 0.1/0.1/[0.1]
```

Question 6:

Transient Graph :

 

Netlist:

```
cmos_inv_tran1
* add a line here include the model file
.INC my_nmos.lib
.INC my_pmos.lib

** Circuit Description **
VDD 2 0 DC 1.8V

* add a line here (pulse source)
Vtran 1 0 PULSE (0 1.8 0 5p 5p 50p 100p)
* add two lines here (NMOS and PMOS instantiation )
** Cmos Inverter
*M4 3 1 2 2 pmos_part1_4 L=0.18u W=20u
*M5 3 1 0 0 nmos_part1_1 L=0.18u W=10u

*** Part 6
** Cmos Inverter With Caps
M6 3 1 2 2 pmos_part1_6 L=0.18u W=20u PD=22u PS=22u AD=9p AS=9p
M7 3 1 0 0 nmos_part1_6 L=0.18u W=10u PD=10.9u PS=10.9u AD=4.5p AS=4.5p

** Analysis Requests **
*add a line here (use transient analysis for two periods)
.TRAN 5p 200p

*Measuring Delay
.MEAS TRAN TRISE
+ TRIG when v(3) = 0.1 CROSS = 1
+ Targ when v(3) = 0.9 CROSS = 1
.END
```

Delay Measurement:

```
SPICE Error Log: C:\Users\marwa\OneDrive\Desktop\Analog Tasks\Lab 3\Ntlists\cmos_inv_tran.log
Circuit: CMOS inverter tran analysis

Instance "m7": Length shorter than recommended for a level 1 MOSFET.
Instance "m6": Length shorter than recommended for a level 1 MOSFET.
Direct Newton iteration for .op point succeeded.

trise=-1.98619e-012 FROM 6.70334e-012 TO 4.71715e-012


Date: Mon Aug 15 14:22:00 2022
Total elapsed time: 0.049 seconds.

tnom = 27
temp = 27
method = modified trap
totiter = 2248
traniter = 2241
tranpoints = 1094
accept = 1081
rejected = 13
matrix size = 5
fillins = 0
solver = Normal
Matrix Compiler1: 150 bytes object code size 0.1/0.1/[0.0]
Matrix Compiler2: off [0.1]/0.1/0.1

3u W=20u
```

PART2:


Question 1 :

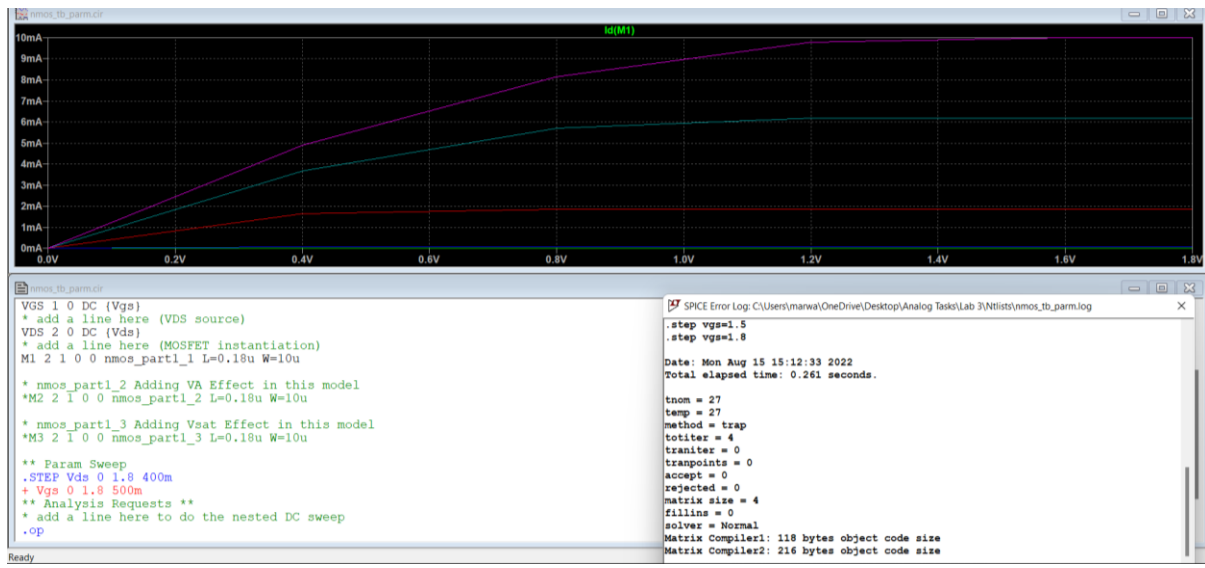


Using Dc Sweep is much faster about 8.5x Faster Than using Parametric Sweeps.

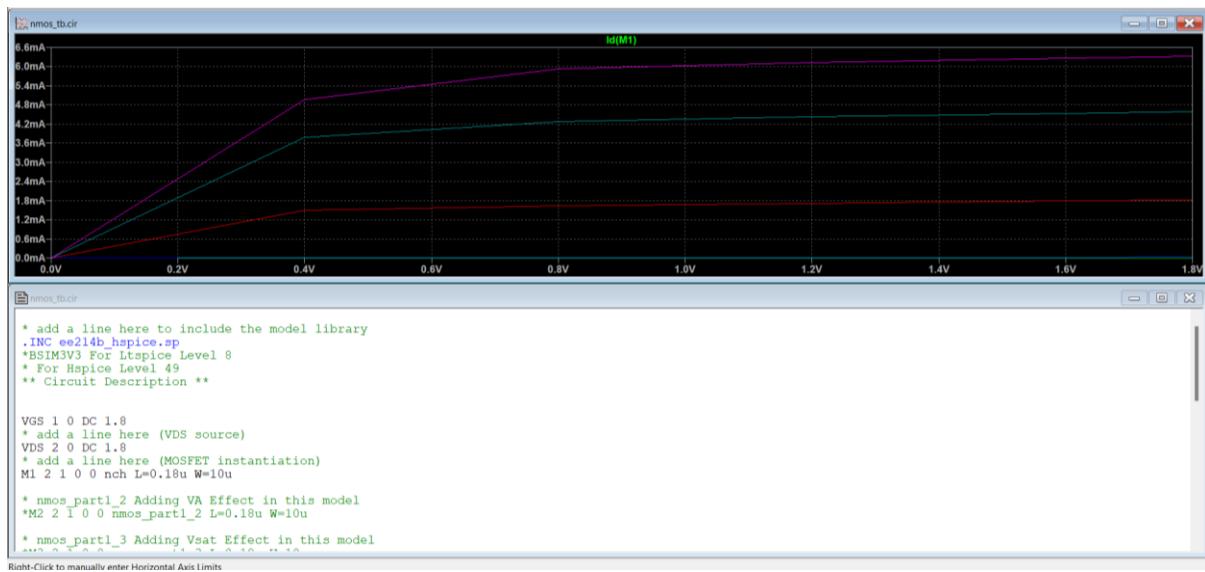Question 2 :

The files uses BSIM3v3 the Level Parameter Must be Set to Level 8 @Ltpspice.



Level 1 Model :

 

Bsim3v3 is more Accurate as it uses more Advanced Models , But Level 1 Uses The Square law which is valid only With Long Channel devices so it didn't give accurate results for our 180nm L Device As Shown.

Question 3 :

```
SPICE Error Log: C:\Users\marwa\OneDrive\Desktop\Analog Tasks\Lab 3\Ntlists\nmos_tb.log
Circuit: NMOS testbench
Ignoring BSIM parameter ACM
Ignoring BSIM parameter HDIF
Ignoring BSIM parameter XL
Ignoring BSIM parameter XW
Error on line 8 : .model nch nmos ( acm = 3 hdif = 0.32e-6 level = 8 version = 3.3
* Unrecognized parameter "cagate" -- ignored
Warning: Pd = 0 is less than W.
Warning: Ps = 0 is less than W.
.OP point found by inspection.
.step vgs=0
.step vgs=0.5
.step vgs=1
.step vgs=1.5
.step vgs=1.8
Date: Mon Aug 15 15:40:59 2022
```

ACM


Area Calculation Method it Describe How to Calculate the area of Drain , Source Changing This will change in The Area of the Device and Capacitance.

HDIF	Length of highly Dopped Diffusion , will change The Capacitance of Source , Drain.
XL	Length for The Masking and Etching Process , It will Effect The Effective length of the Device.
XW	Width for The Masking and Etching Process , It will Effect The Effective Width of the Device.

This BSIM Parameters are not supported in Itspice , if it was supported the area modifications will effect the caps that effects the speed of the transistor , and effective width may Effect the current.

Question 4 :

FO4 Graph :

 

FO4 Netlist :

```
cmos_inv_tran_fo4.cir
.SUBCKT Cmos_Inv 3 2 1 PARAMS: MULT=1
*
*      / /
*      / / OUT
*      / / Supply
*      / / In
* Mosfets Init
M1 1 3 2 2 pch (L=0.18u W=20u M={MULT} )
M2 1 3 0 0 nch (L=0.18u W=10u M={MULT} )
.ENDS Cmos_Inv
* Supply Voltage
Vs VDD 0 1.8

* Init The 5 Invertors

*Shaping Input Inverter
X_I1 1 VDD 2 Cmos_Inv PARAMS: MULT={4**0}

*Shaping Input Inverter
X_I2 2 VDD 3 Cmos_Inv PARAMS: MULT={4**1}

*Test Inverter
X_I3 3 VDD 4 Cmos_Inv PARAMS: MULT={4**2}


*Loading Invertor
X_I4 4 VDD 5 Cmos_Inv PARAMS: MULT={4**3}

*Loading Input Inverter
X_I5 5 VDD 6 Cmos_Inv PARAMS: MULT={4**4}
* Input Voltage
* Transient for cmos
Vtran 1 0 PULSE (0 1.8 0 5p 5p 1n 2n)
.TRAN 1n 4n

* Measuring Delay
.MEAS TRAN TRISE
+ TRIG when v(3) = 0.9 CROSS = 1
+ Targ when v(4) = 0.9 CROSS = 1
```

Question 5 :

Measuring Delay :

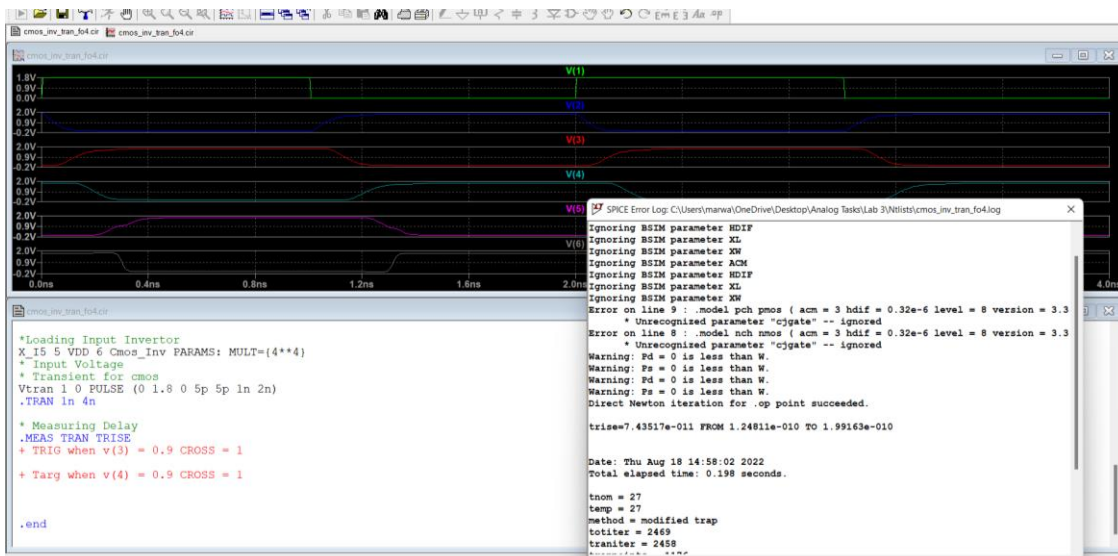

Delay/Lamda = 826.13E-6

Delay For 65nm Tech = 26.8492p